



SVES ESTD 1992
Sri Vishnu Educational Society




in partnership with
Mr. Alan Rux - University of Massachusetts
presents

Oscillators , Timers & Analog Discovery Kit


lecture 2

555 Timer

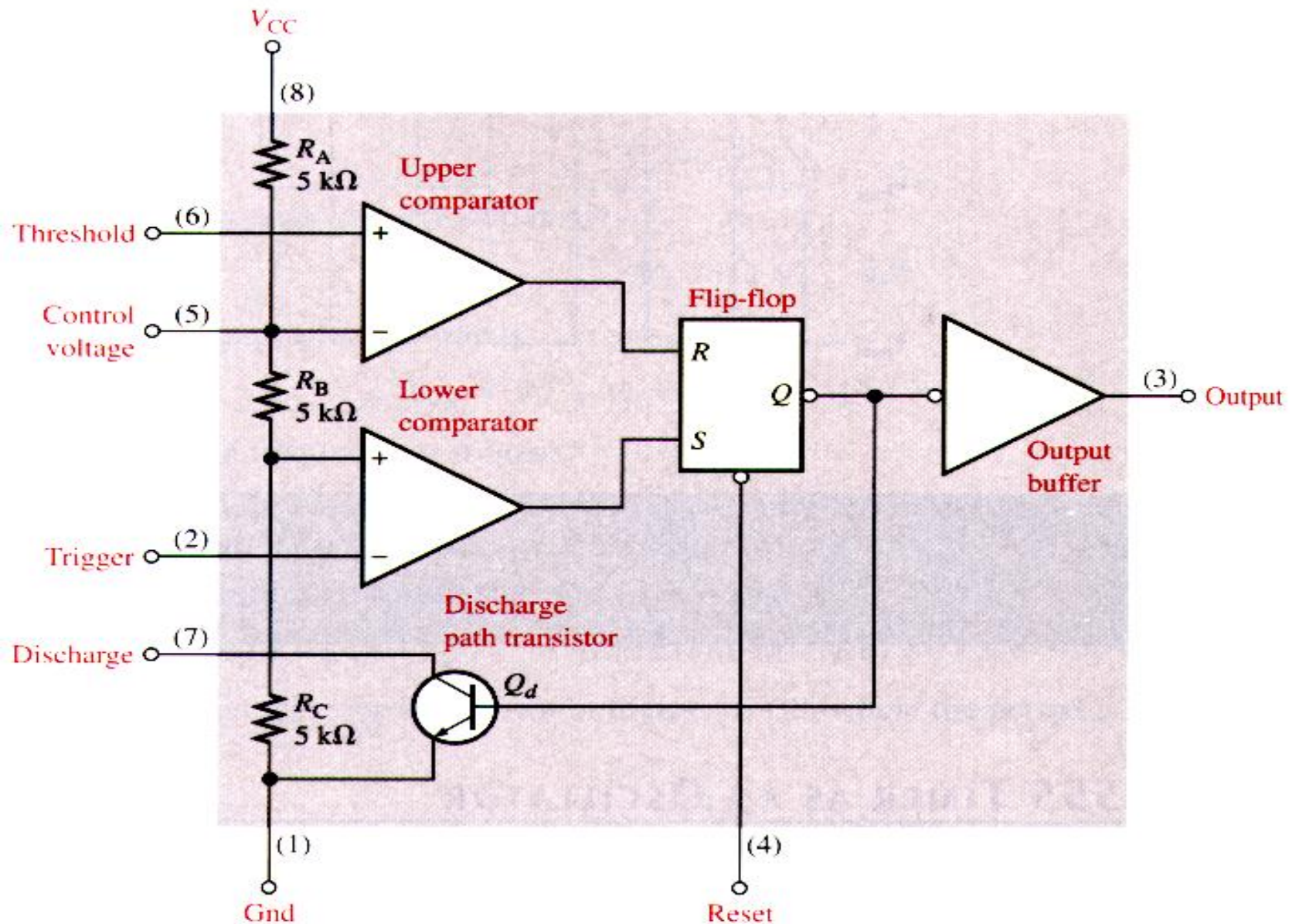

555 Timer Modes

Monostable (one-shot)

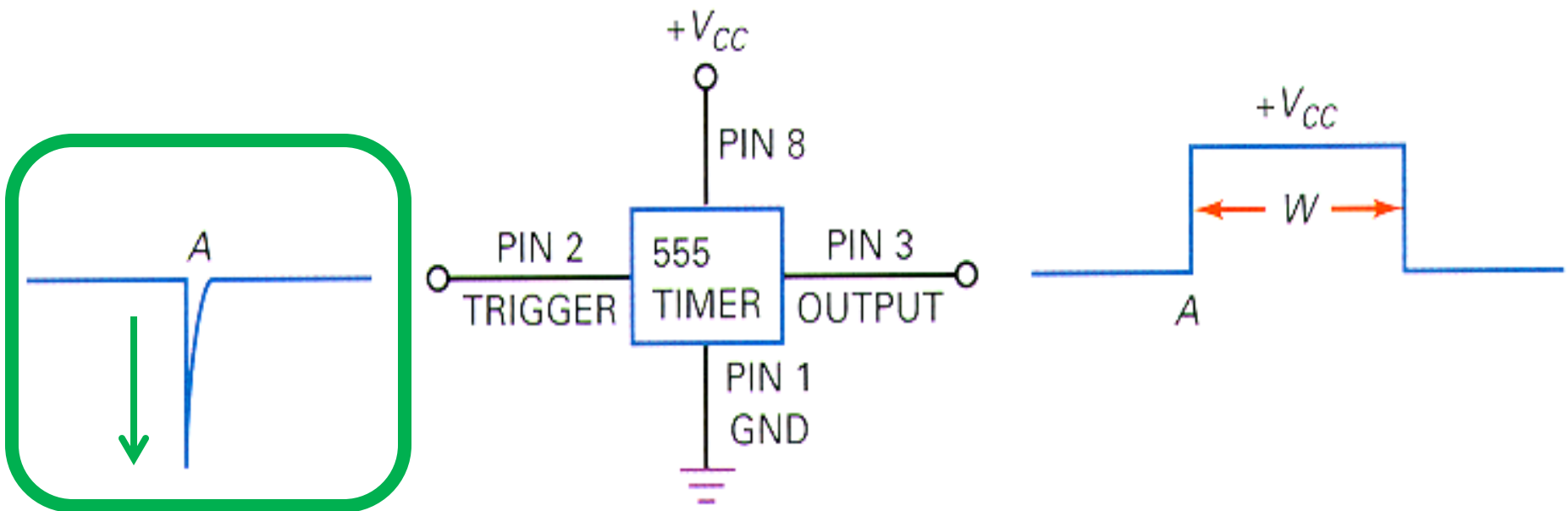


Negative trigger  Pulse

Monostable (one-shot)

- have only **ONE** stable state (hence their name: “Mono”), and produce a **single output pulse** when it is **triggered externally**
- return back to their first original and stable state after a period of time determined by the time constant of the RC coupled circuit
- One main disadvantage of “monostable multivibrators” is that the time between the application of the next trigger pulse has to be greater than the preset RC time constant of the circuit to allow the capacitor time to charge and discharge

Monostable Timer Circuit

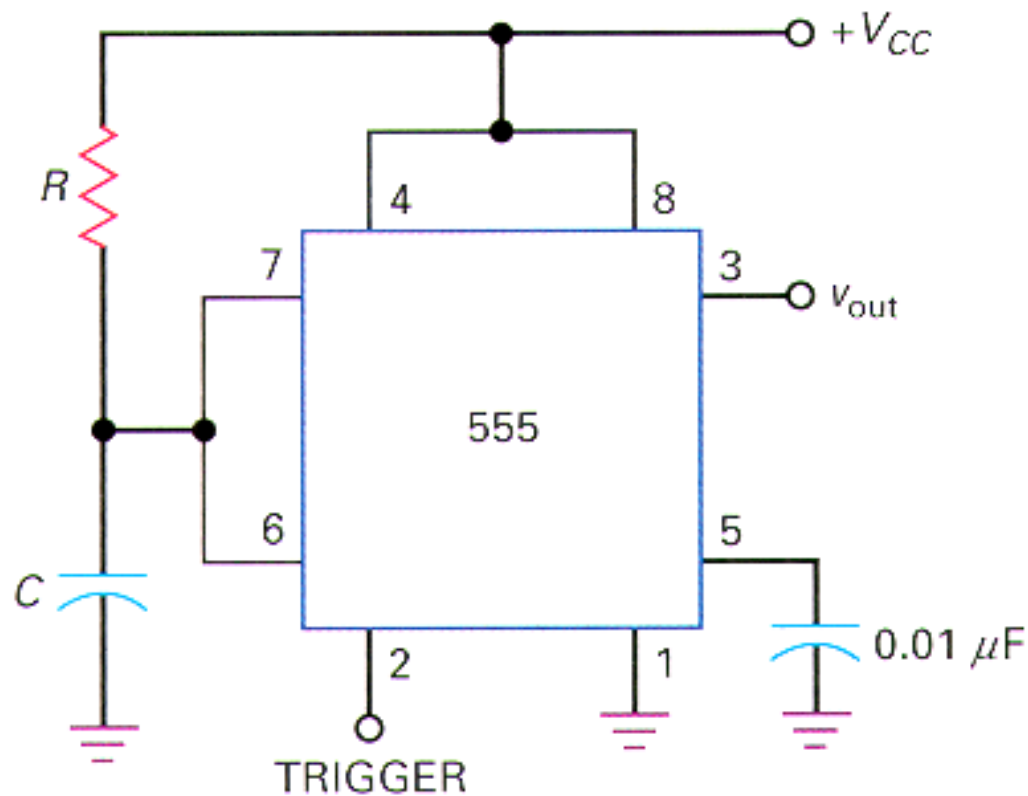


$$\text{UTP} = \frac{2V_{\text{CC}}}{3}$$


$$\text{LTP} = \frac{V_{\text{CC}}}{3}$$

$$W = 1.1RC$$

555 Timer

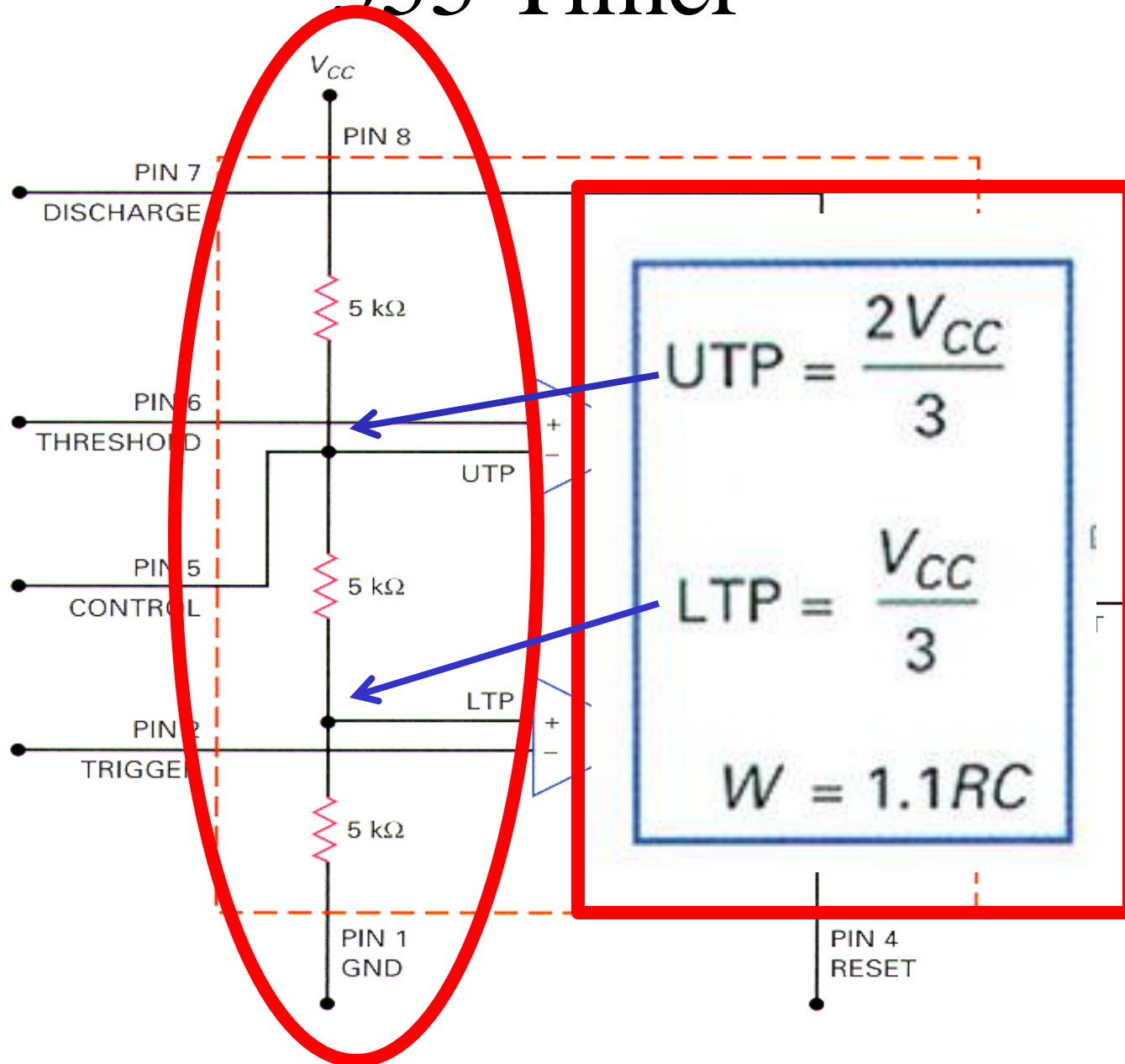


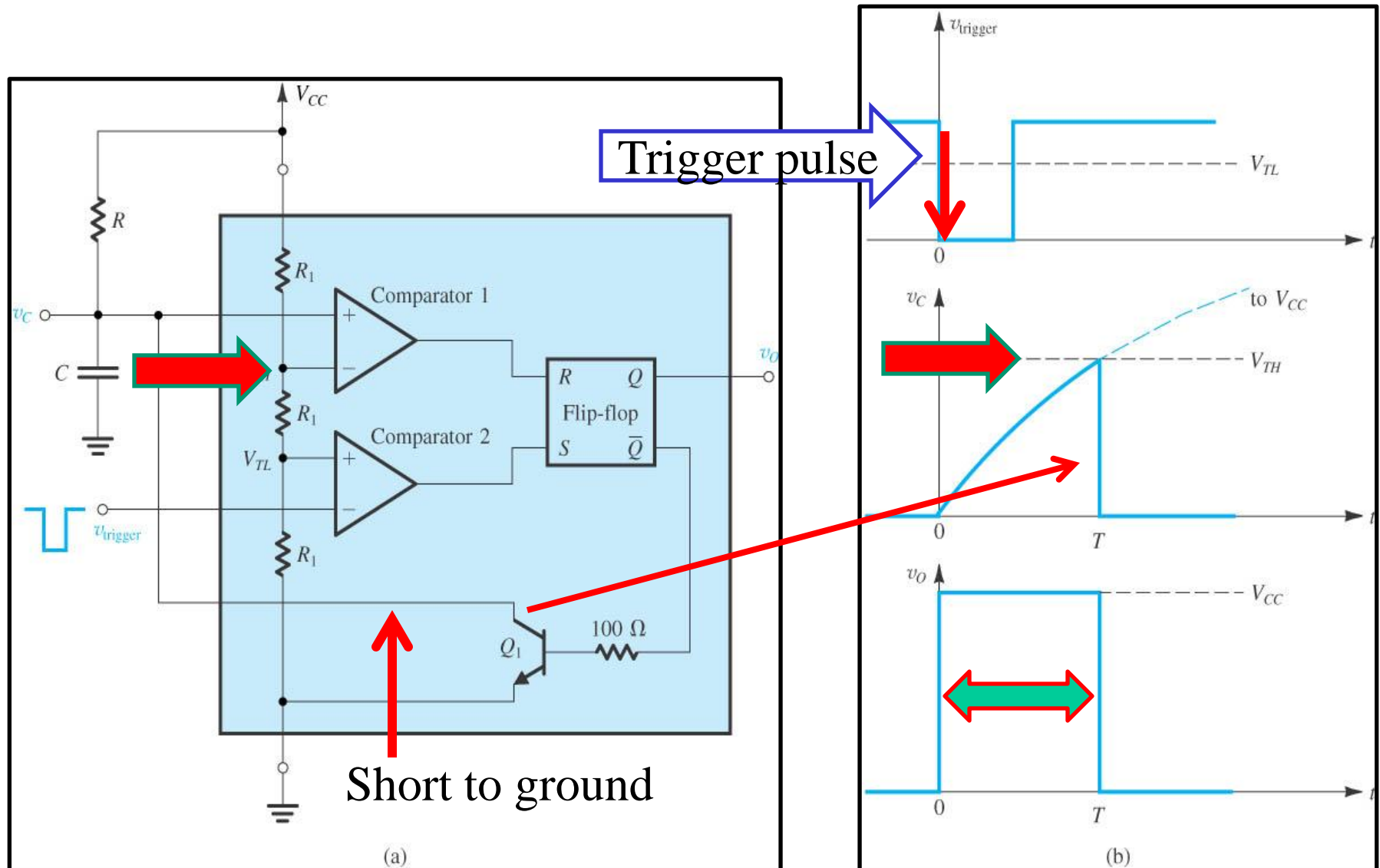(a) The 555 timer connected to implement a monostable multivibrator. **(b)** Waveforms of the circuit in (a).




(pulse width) **$W = 1.1 RC$**

capacitor voltage in an RC circuit

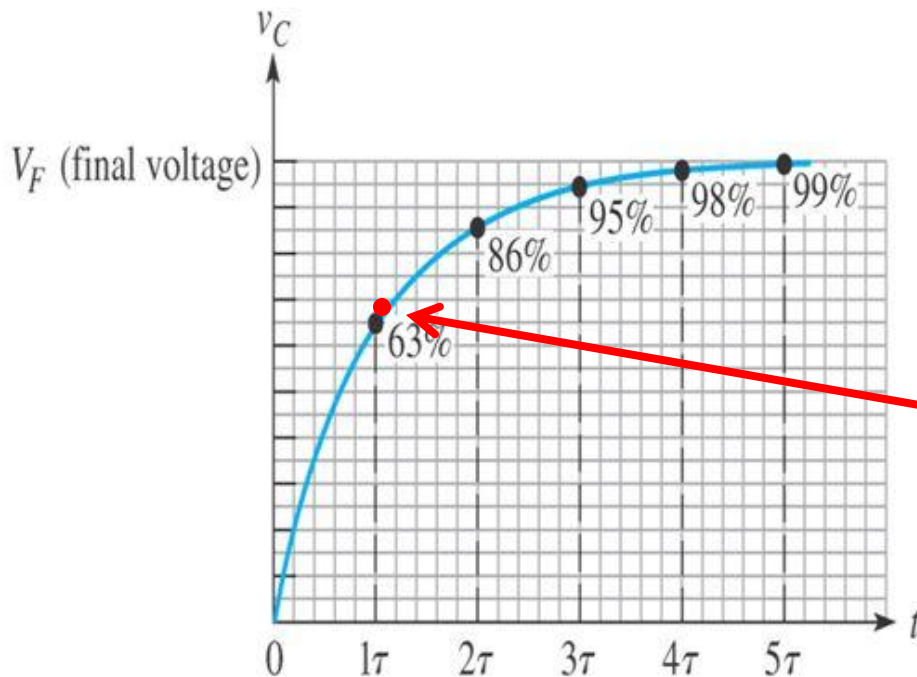

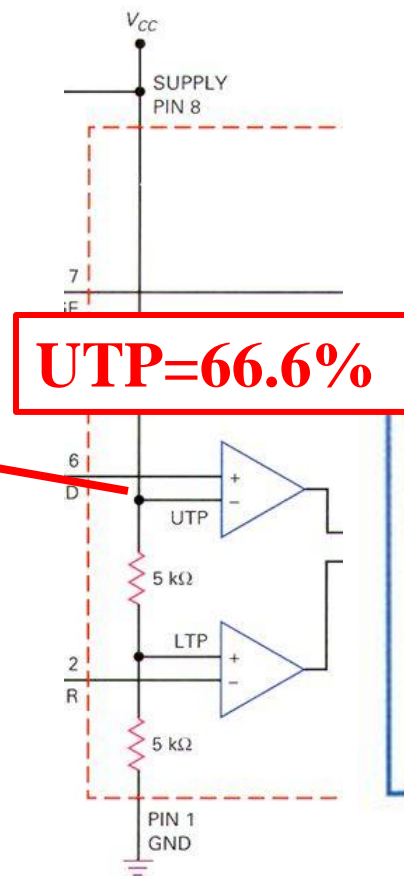(a) Charging curve with percentages of final voltage



UTP=66.6%

$$UTP = \frac{2V_{CC}}{3}$$


$$LTP = \frac{V_{CC}}{3}$$


$$W = 1.1RC$$

1 RC Time = 63%

Monostable Operation

pulse width
 $W = 1.1RC$

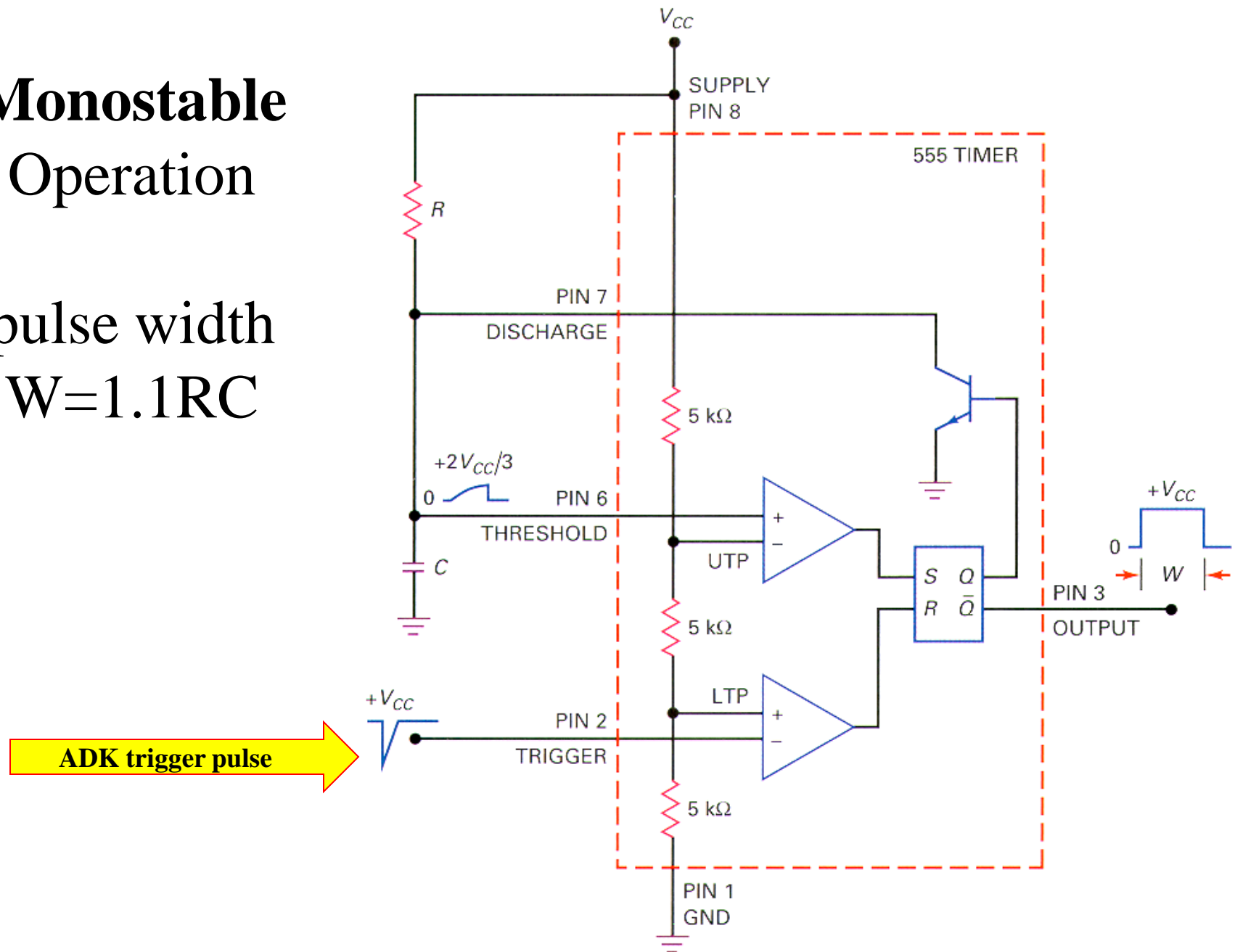


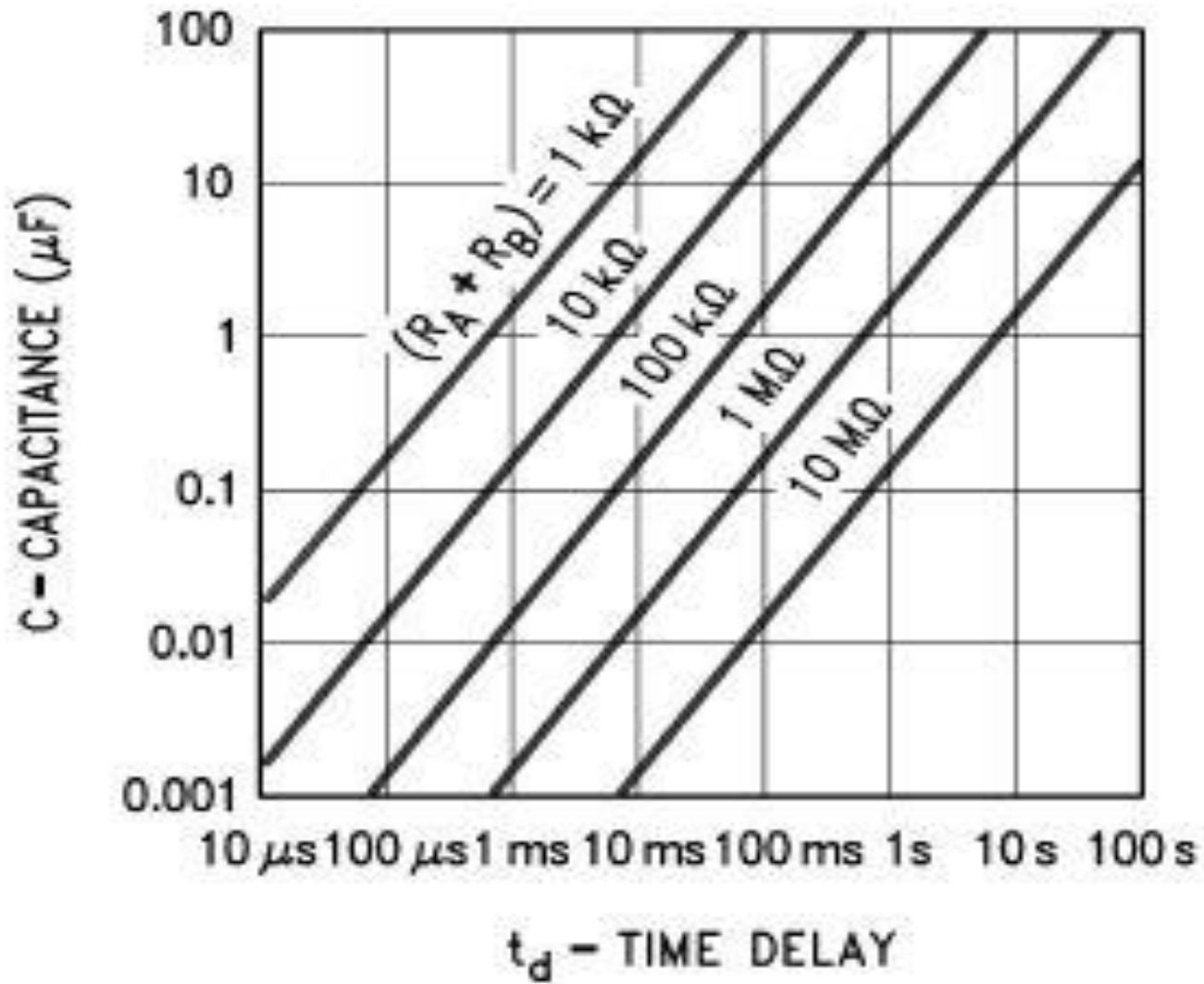

PULSE WIDTH Table



PULSE WIDTH MODULATOR

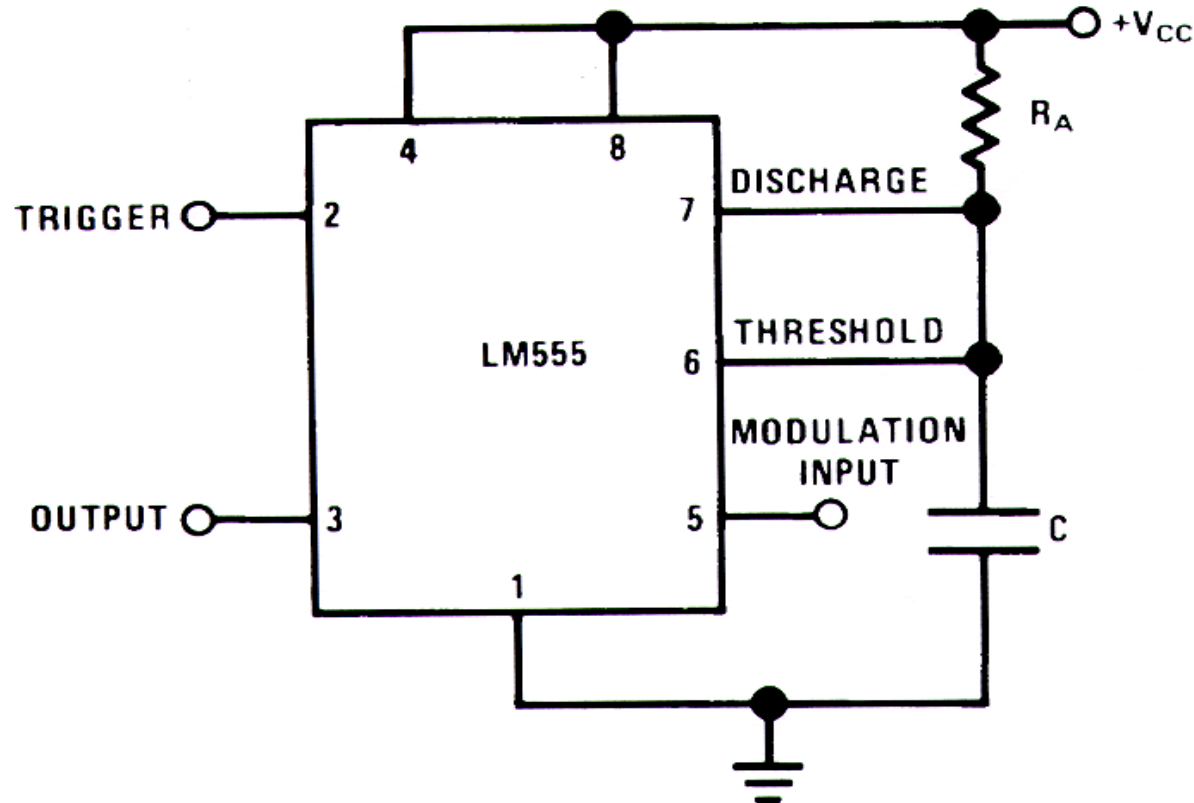When the timer is connected in the monostable mode and triggered with a continuous pulse train, the output pulse width can be modulated by a signal applied to pin 5. *Figure 8* shows the circuit, and in *Figure 9* are some waveform examples.




Pulse Width Modulation using LM555

Pulse Width Modulator

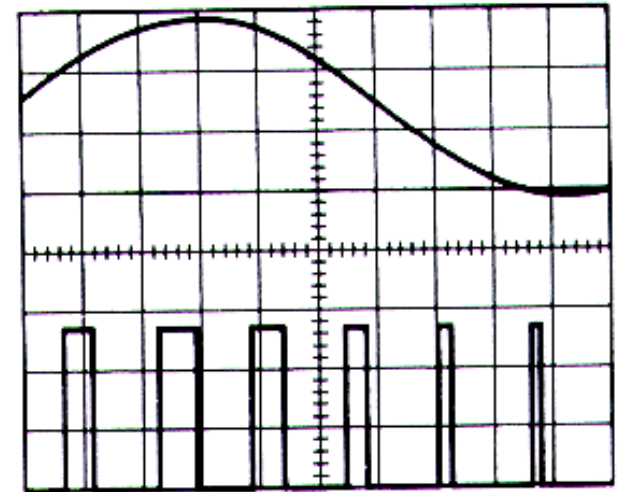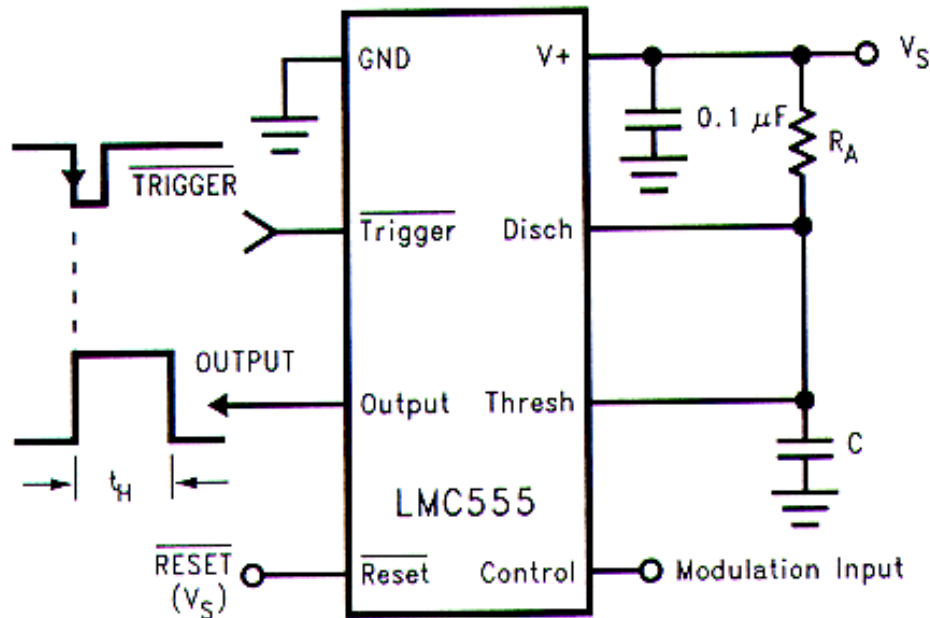

00866915

Pulse - Width Modulator

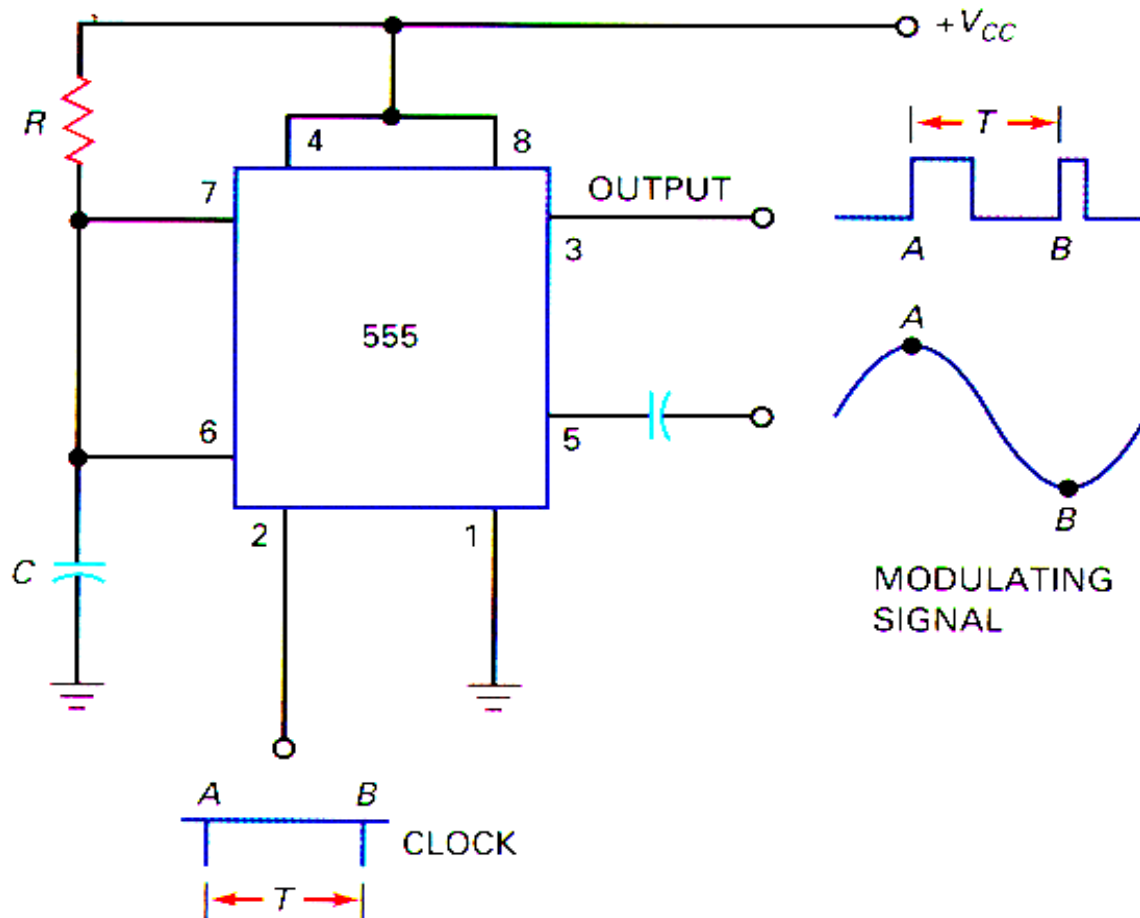


$$T = \frac{1}{f_{\text{clock}}}$$

$$UTP = \frac{2V_{CC}}{3} + V_{\text{mod}}$$


$$W = -RC \ln \left(1 - \frac{UTP}{V_{CC}} \right)$$

$$D = \frac{W}{T}$$


Pulse Width Modulation

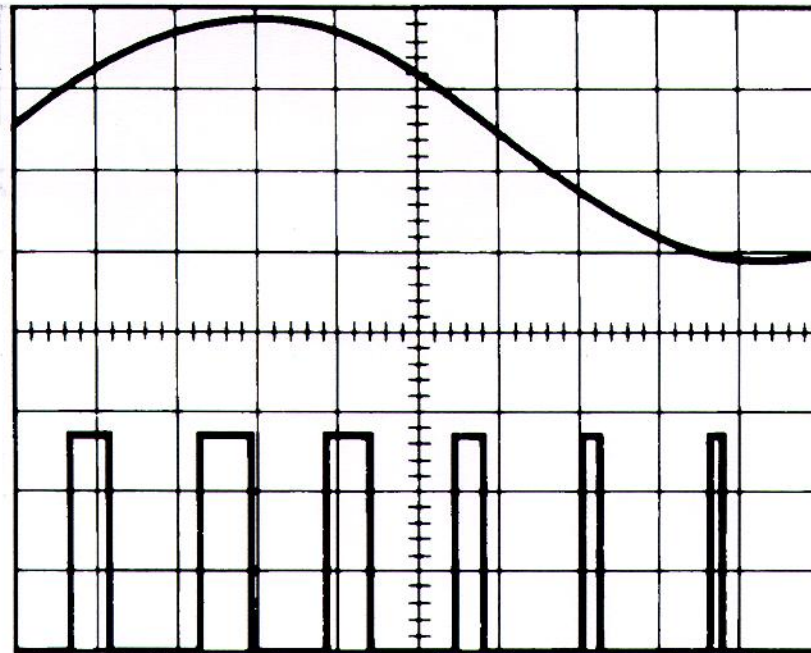

Pulse Width Modulation

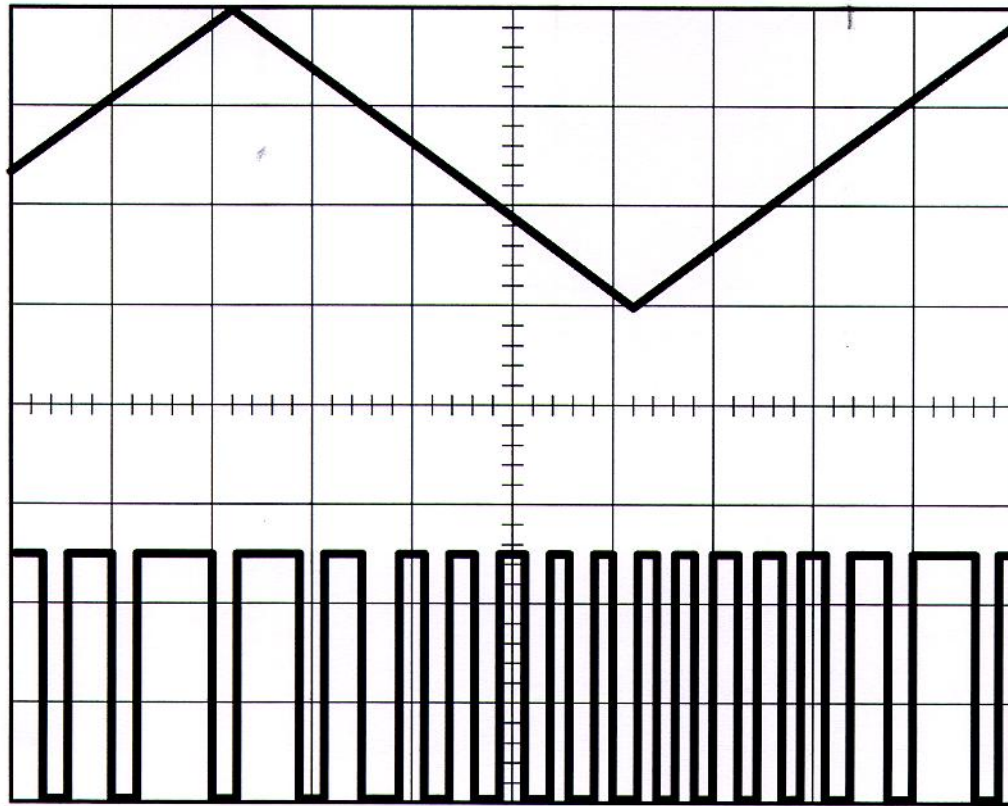

Pulse - Position Modulator

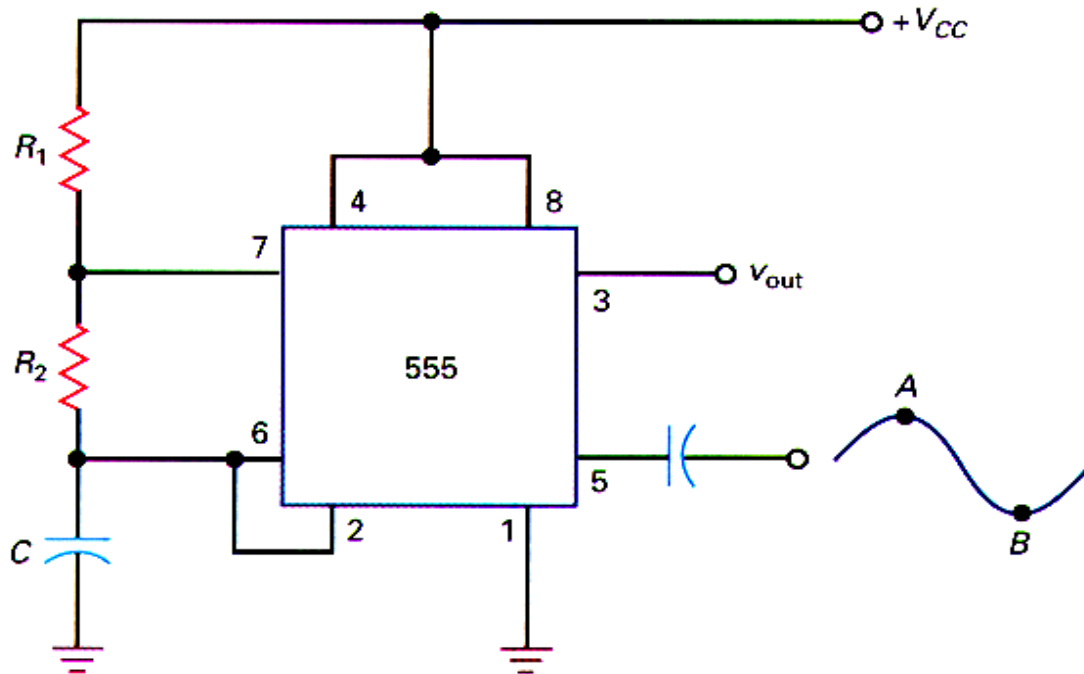


(a)

$$UTP = \frac{2V_{CC}}{3} + v_{mod}$$

$$W = -(R_1 + R_2)C \ln \frac{V_{CC} - UTP}{V_{CC} - 0.5UTP}$$

$$T = W + 0.693R_2C$$

$$Space = 0.693R_2C$$

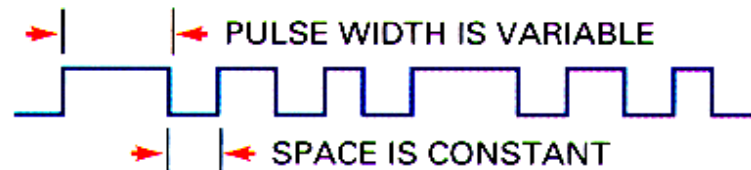

T I Data Sheet

http://www.ti.com/lit/ds/symlink/lm555.pdf

File Edit Go to Favorites Help

Downloads Google Apply for Funding skf NGO consultants - Gra... Echo360 RSS Class Feeds comcast.net-jsessionid=L... exchange.uml.edu-owa-a...

1 / 21 75%

Tools

Bookmarks

- FEATURES
- Applications
- DESCRIPTION
- Absolute Maximum Ratings
- Electrical Characteristics
- Typical Performance Characteristics
- Applications Information
- Revision History

TEXAS INSTRUMENTS

LM555

www.ti.com SNAS549C – FEBRUARY 2000 – REVISED MARCH 2013

LM555 Timer

Check for Samples: LM555

FEATURES	DESCRIPTION
<ul style="list-style-type: none">• Direct Replacement for SE555/NE555• Timing from Microseconds through Hours• Operates in Both Astable and Monostable Modes• Adjustable Duty Cycle• Output Can Source or Sink 200 mA• Output and Supply TTL Compatible• Temperature Stability Better than 0.005% per °C• Internally On and Internally Off Output Available in 8-pin VSSOP Package	<p>The LM555 is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired. In the time delay mode of operation, the time is precisely controlled by one external resistor and capacitor. For astable operation as an oscillator, the free running frequency and duty cycle are accurately controlled with two external resistors and one capacitor. The circuit may be triggered and reset on falling waveforms, and the output circuit can source or sink up to 200mA or drive TTL circuits.</p>

APPLICATIONS

- Precision Timing
- Pulse Generation
- Sequential Timing
- Time Delay Generation
- Pulse Width Modulation
- Pulse Position Modulation
- Linear Ramp Generator

Schematic Diagram

Please be aware that an important notice concerning availability, standard warranty, and use in critical applications of Texas Instruments semiconductor products and disclaimers thereto appears at the end of this data sheet. All trademarks are the property of their respective owners.

PRODUCTION DATA information is current as of publication date. Products conform to specifications per the terms of the Texas Instruments standard warranty. The quality management system is ISO 9001:2008 certified.

Copyright © 2000–2013, Texas Instruments Incorporated

LM555 Timer

Check for Samples: [LM555](#)

FEATURES

- Direct Replacement for SE555/NE555
- Timing from Microseconds through Hours
- Operates in Both Astable and Monostable Modes
- Adjustable Duty Cycle
- Output Can Source or Sink 200 mA
- Output and Supply TTL Compatible
- Temperature Stability Better than 0.005% per °C
- Normally On and Normally Off Output
- Available in 8-pin VSSOP Package

APPLICATIONS

- Precision Timing
- Pulse Generation
- Sequential Timing
- Time Delay Generation
- Pulse Width Modulation
- Pulse Position Modulation
- Linear Ramp Generator

DESCRIPTION

The LM555 is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired. In the time delay mode of operation, the time is precisely controlled by one external resistor and capacitor. For astable operation as an oscillator, the free running frequency and duty cycle are accurately controlled with two external resistors and one capacitor. The circuit may be triggered and reset on falling waveforms, and the output circuit can source or sink up to 200mA or drive TTL circuits.

T I Data Sheet

APPLICATIONS

- Precision Timing
- Pulse Generation
- Sequential Timing
- Time Delay Generation
- Pulse Width Modulation
- Pulse Position Modulation
- Linear Ramp Generator

T I Data Sheet

http://www.ti.com/lit/ds/symlink/lm555.pdf

File Edit Go to Favorites Help

Downloads Google Apply for Funding skf NGO consultants - Gra... Echo360 RSS Class Feeds comcast.net-jsessionid=L... exchange.uml.edu-owa-a...

1 / 21 75%

Bookmarks

FEATURES

Applications

DESCRIPTION

Absolute Maximum Ratings

Electrical Characteristics

Typical Performance Characteristics

Applications Information

Revision History

TEXAS INSTRUMENTS

LM555

www.ti.com

SNAS548C—FEBRUARY 2000—REVISED MARCH 2013

LM555 Timer

Check for Samples: LM555

FEATURES

- Direct Replacement for SE555/NE555
- Timing from Microseconds through Hours
- Operates in Both Astable and Monostable Modes
- Adjustable Duty Cycle
- Output Can Source or Sink 200 mA
- Output and Supply TTL Compatible
- Temperature Stability Better than 0.005% per °C
- Normally On and Normally Off Output
- Available in 8-pin VSSOP Package

DESCRIPTION

The LM555 is a highly stable device for generating accurate time delays or oscillation. Additional terminals are provided for triggering or resetting if desired. In the time delay mode of operation, the time is precisely controlled by one external resistor and capacitor. For astable operation as an oscillator, the free running frequency and duty cycle are accurately controlled with two external resistors and one capacitor. The circuit may be triggered and reset on falling waveforms, and the output circuit can source or sink up to 200mA or drive TTL circuits.

APPLICATIONS

- Precision Timing
- Pulse Generation
- Sequential Timing
- Time Delay Generation
- Pulse Width Modulation
- Pulse Position Modulation
- Linear Ramp Generator

Schematic Diagram

TI Data Sheet page 9 & 10

PULSE WIDTH MODULATOR

When the timer is connected in the monostable mode and triggered with a continuous pulse train, the output pulse width can be modulated by a signal applied to pin 5. Figure 19 shows the circuit, and in Figure 20 are some waveform examples.

LM555


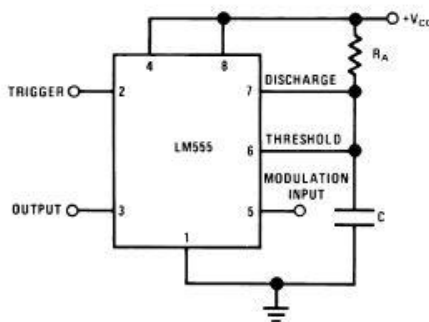


Figure 19. Pulse Width Modulator

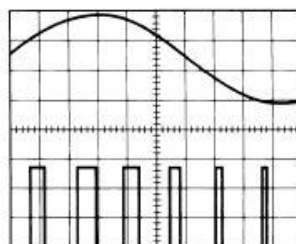

PULSE WIDTH MODULATOR

When the timer is connected in the monostable mode and triggered with a continuous pulse train, the output pulse width can be modulated by a signal applied to pin 5. Figure 19 shows the circuit, and in Figure 20 are some waveform examples.


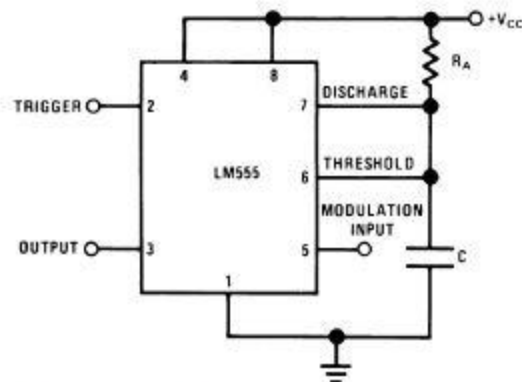


Figure 19. Pulse Width Modulator

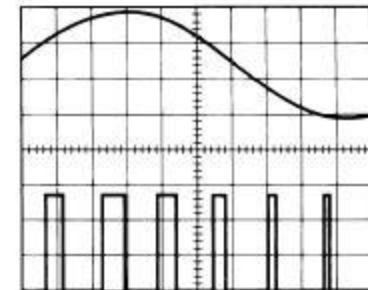$V_{CC} = 5V$
 $TIME = 0.2 \text{ ms/DIV.}$
 $R_A = 9.1k\Omega$
 $C = 0.01\mu F$



Top Trace: Modulation 1V/Div.
Bottom Trace: Output Voltage 2V/Div.

Figure 20. Pulse Width Modulator

T I Data Sheet page 10

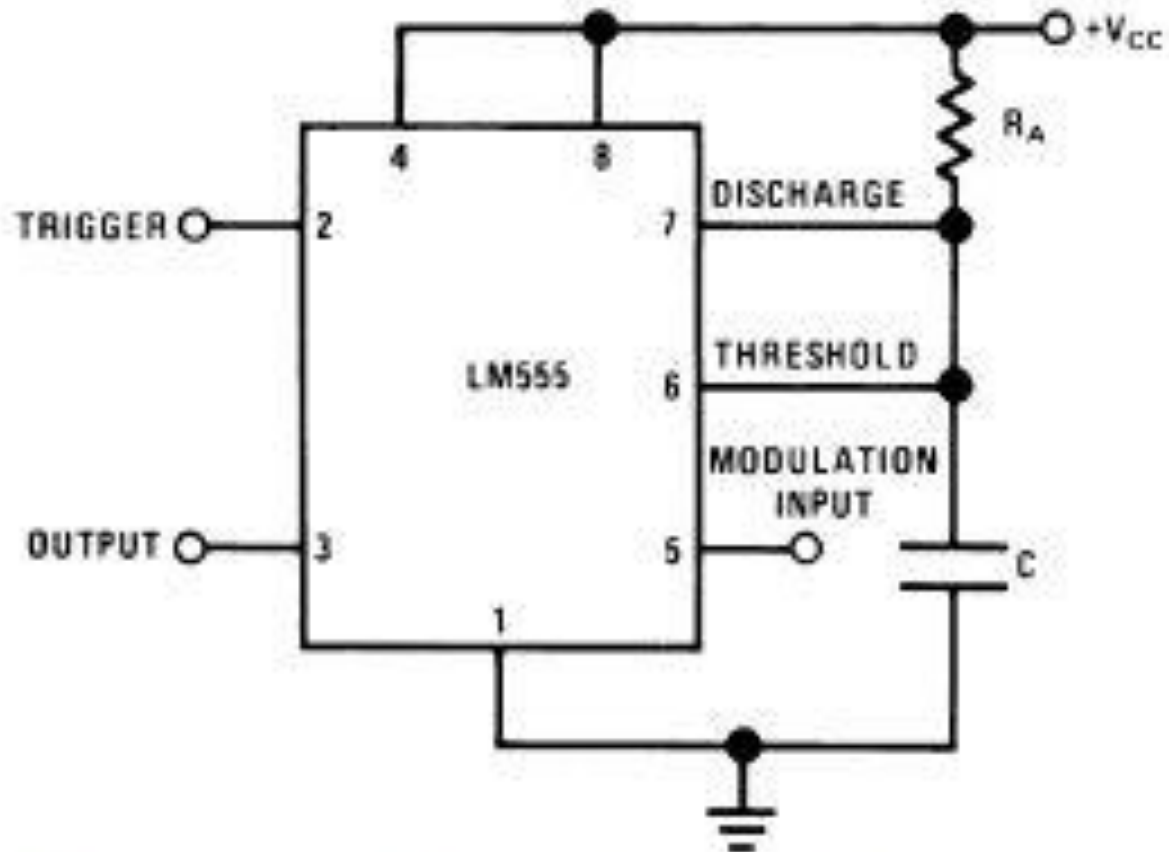



Figure 19. Pulse Width Modulator

$$F = 1 / T$$

$$F = 1 / .3\text{ms}$$

$$F = 3,333.3 \text{ Hz}$$


$$F = 3.3 \text{ kHz}$$

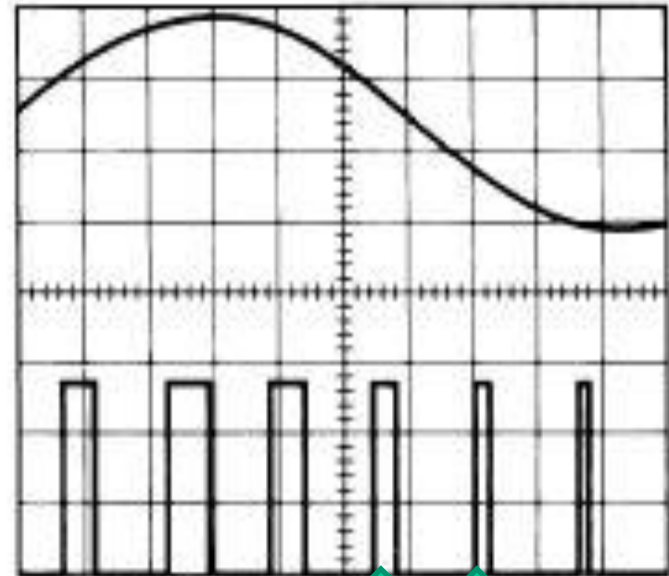

$V_{CC} = 5\text{V}$
 $\text{TIME} = 0.2 \text{ ms/DIV.}$
 $R_A = 9.1\text{k}\Omega$
 $C = 0.01\mu\text{F}$

Top Trace: Modulation 1V/Div.
Bottom Trace: Output Voltage 2V/Div.

Figure 20. Pulse Width Modulator

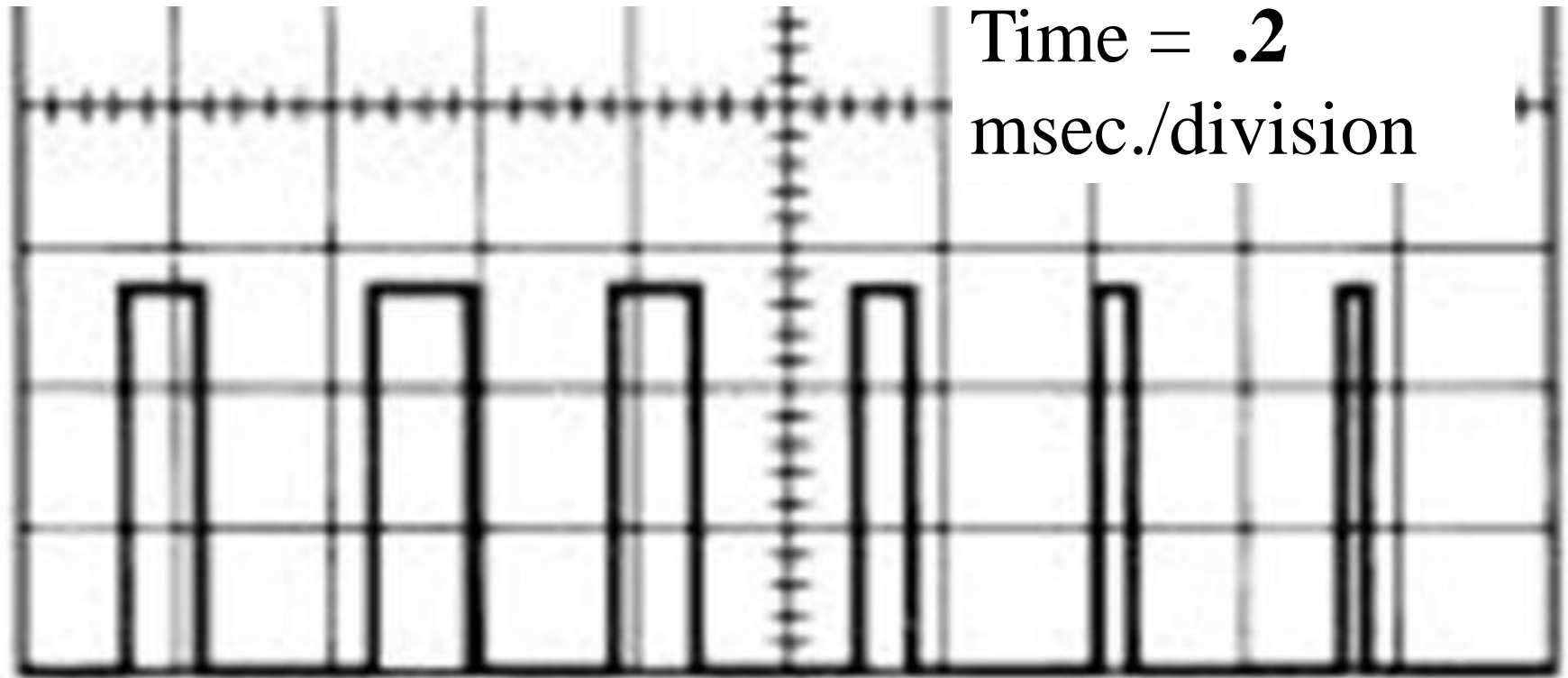

on 1V/Div.

out Voltage 2V/Div.

Fairchild Data Sheet



January 2013

LM555 Single Timer

Features

- High-Current Drive Capability: 200 mA
- Adjustable Duty Cycle
- Temperature Stability of 0.005%/°C
- Timing From μs to Hours
- Turn off Time Less Than 2 μs

Applications

- Precision Timing
- Pulse Generation
- Delay Generation
- Sequential Timing

Description

The LM555 is a highly stable controller capable of producing accurate timing pulses. With a monostable operation, the delay is controlled by one external resistor and one capacitor. With astable operation, the frequency and duty cycle are accurately controlled by two external resistors and one capacitor.

8-DIP



8-SOIC

LM555 — Single Timer

Fairchild Data Sheet

4. Pulse Width Modulation

The timer output waveform may be changed by modulating the control voltage applied to the timer's pin 5 and changing the reference of the timer's internal comparators. Figure 10 illustrates the pulse width modulation circuit. When the continuous trigger pulse train is applied in the monostable mode, the timer output width is modulated according to the signal applied to the control terminal. Sine wave, as well as other waveforms, may be applied as a signal to the control terminal. Figure 11 shows the example of pulse width modulation waveform.

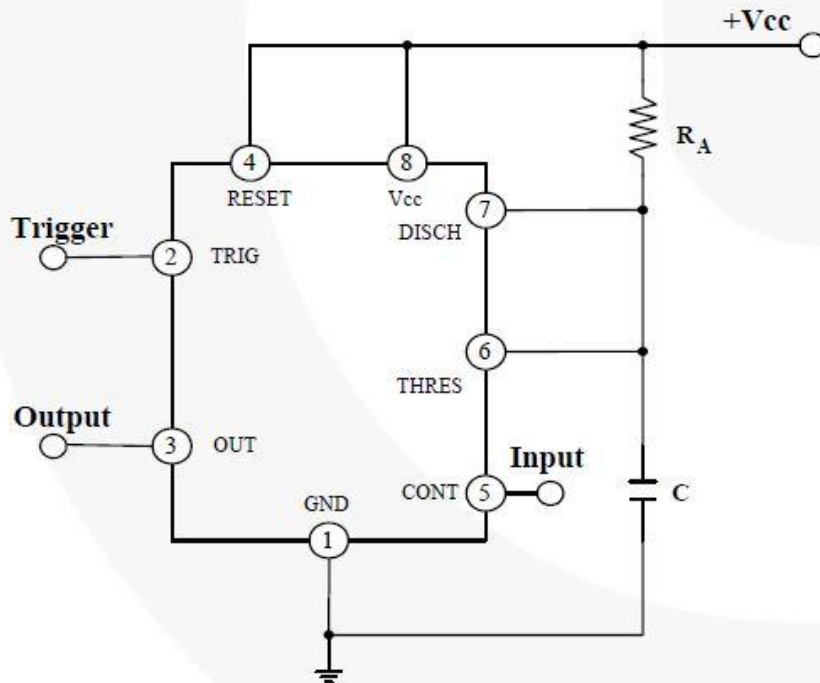


Figure 10. Circuit for Pulse Width Modulation

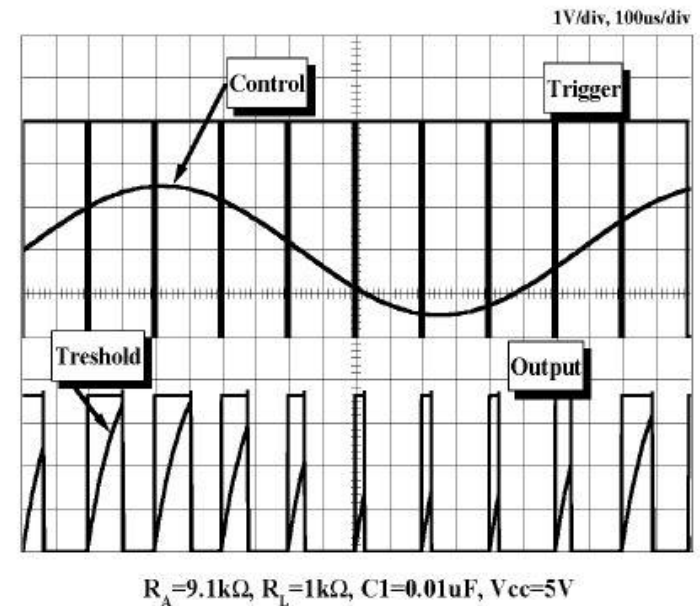


Figure 11. Waveforms of Pulse Width Modulation

Fairchild Data Sheet

4. Pulse Width Modulation

The timer output waveform may be changed by modulating the control voltage applied to the timer's pin 5 and changing the reference of the timer's internal comparators. Figure 10 illustrates the pulse width modulation circuit. When the continuous trigger pulse train is applied in the monostable mode, the timer output width is modulated according to the signal applied to the control terminal. Sine wave, as well as other waveforms, may be applied as a signal to the control terminal. Figure 11 shows the example of pulse width modulation waveform.

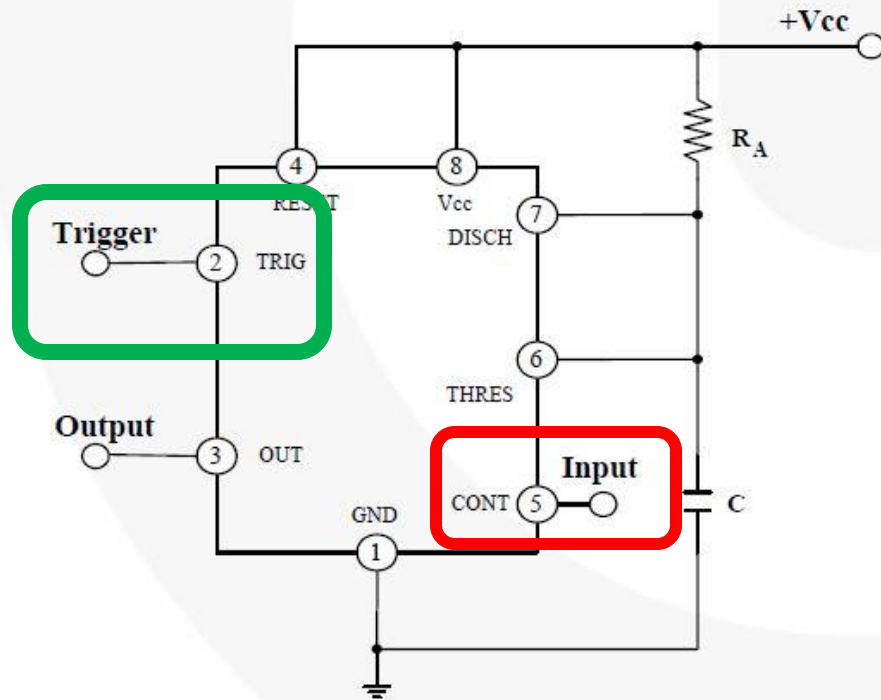


Figure 10. Circuit for Pulse Width Modulation


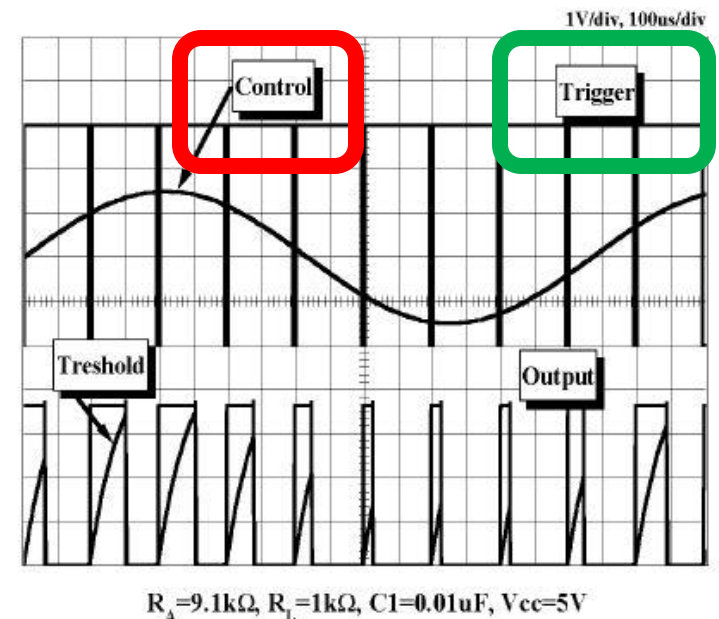




Figure 11. Waveforms of Pulse Width Modulation

PULSE WIDTH MODULATOR

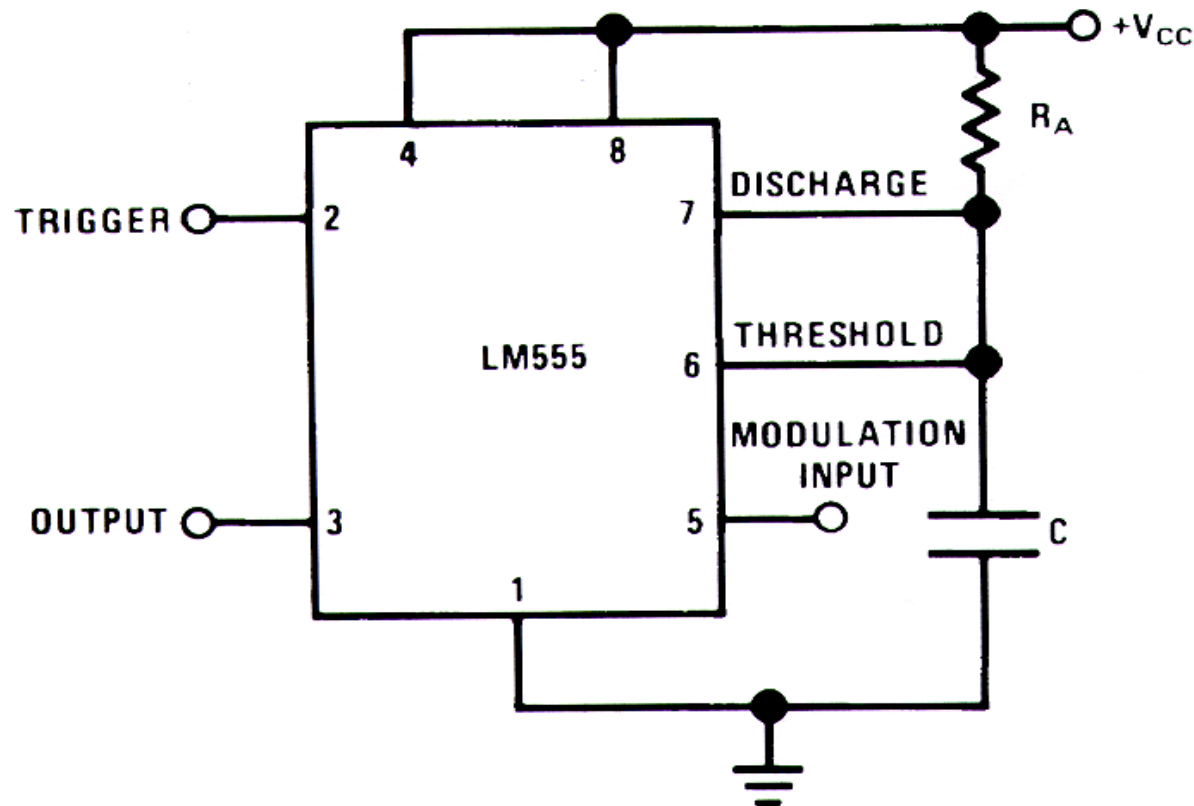
When the timer is connected in the monostable mode and triggered with a continuous pulse train, the output pulse width can be modulated by a signal applied to pin 5. *Figure 8* shows the circuit, and in *Figure 9* are some waveform examples.



Control pin 5

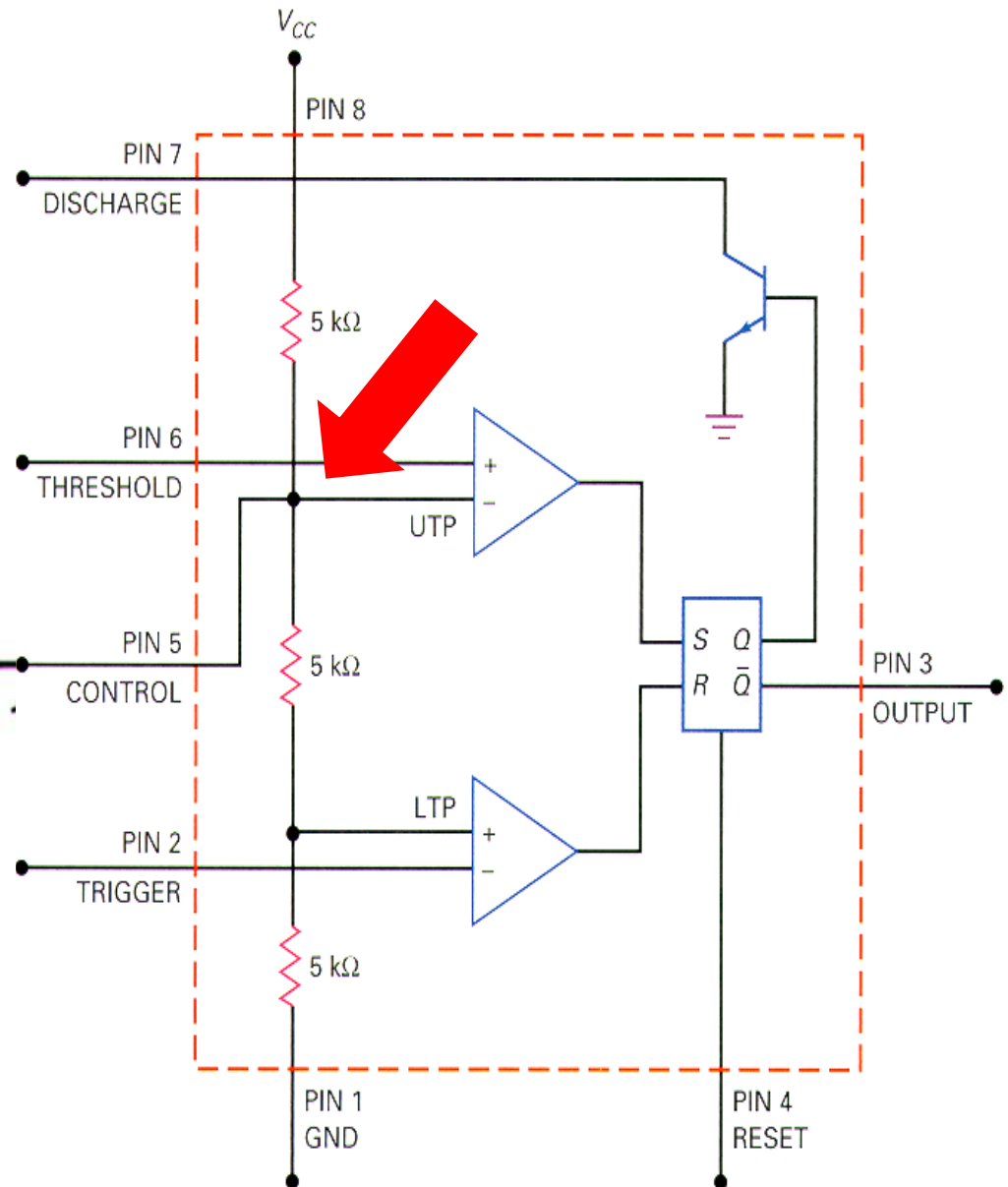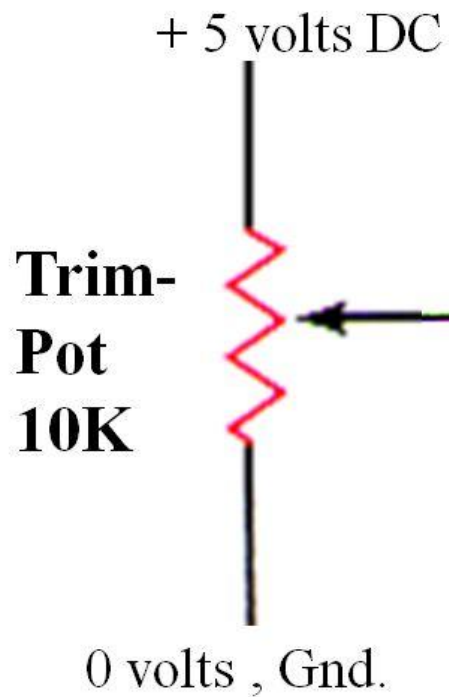

Pulse - Width Modulator

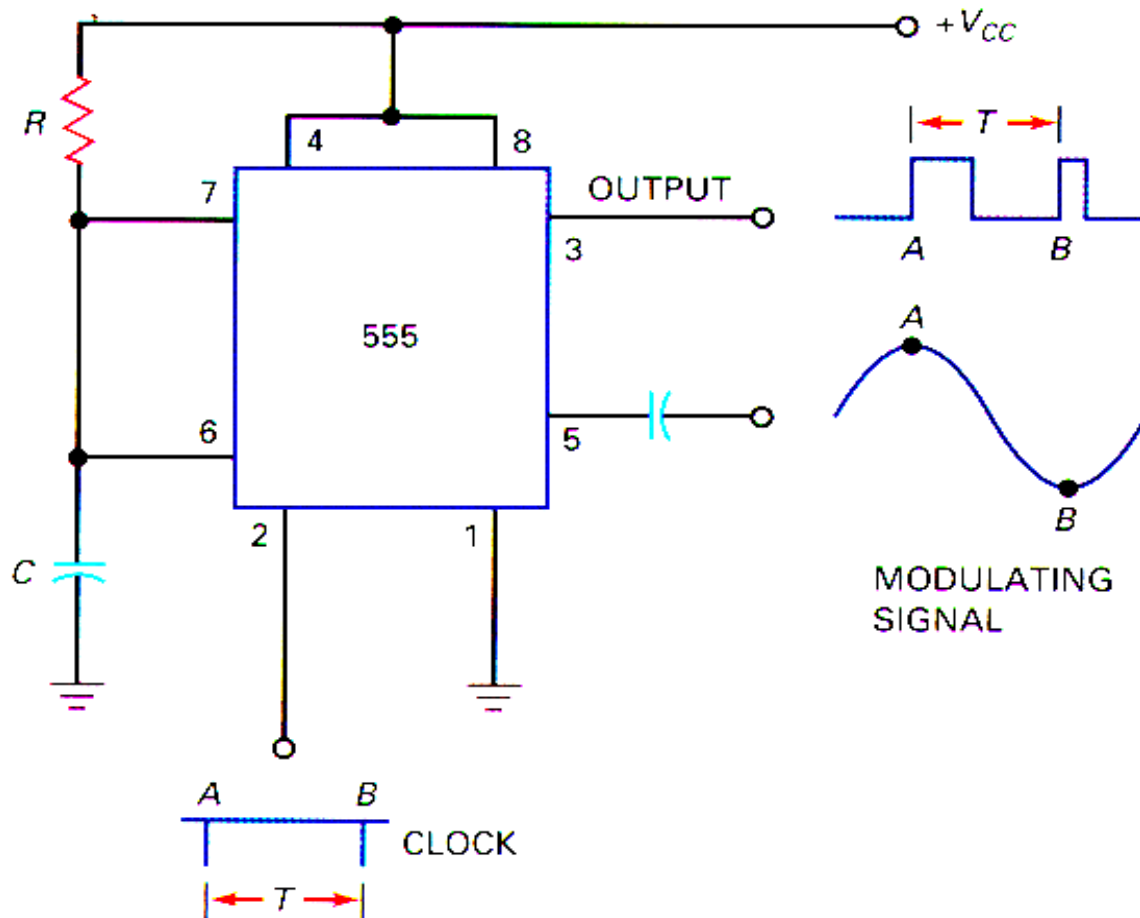


$$T = \frac{1}{f_{\text{clock}}}$$

$$UTP = \frac{2V_{CC}}{3} + V_{\text{mod}}$$

$$W = -RC \ln \left(1 - \frac{UTP}{V_{CC}} \right)$$

$$D = \frac{W}{T}$$

Pulse Width Modulation


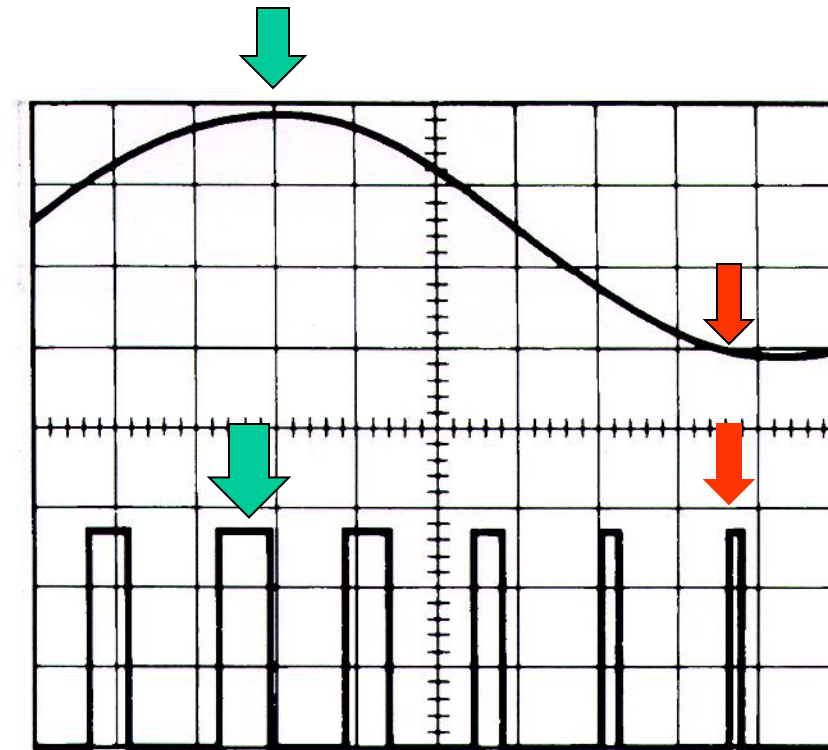


The higher the modulation voltage the wider the pulse

The lower the modulation voltage the narrower the pulse


Pulse Width Modulation using LM555

Pulse Width Modulator

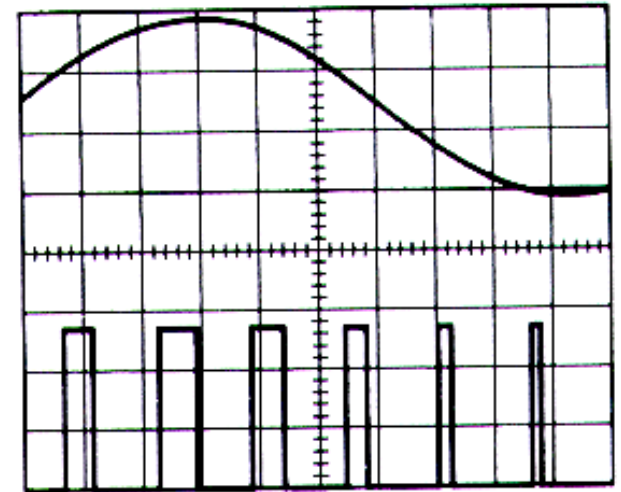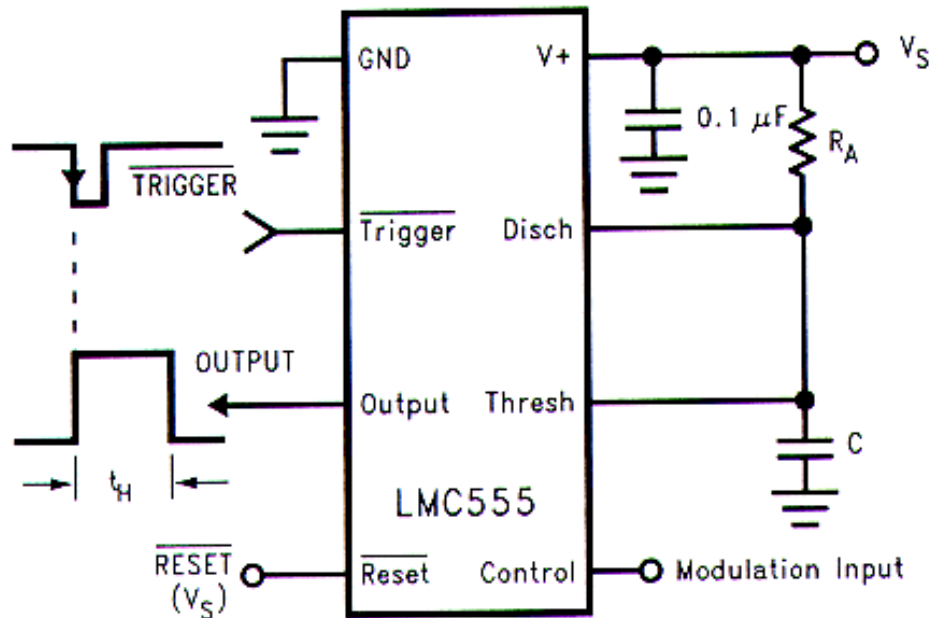

00866915

“Lamp Driver Circuit”

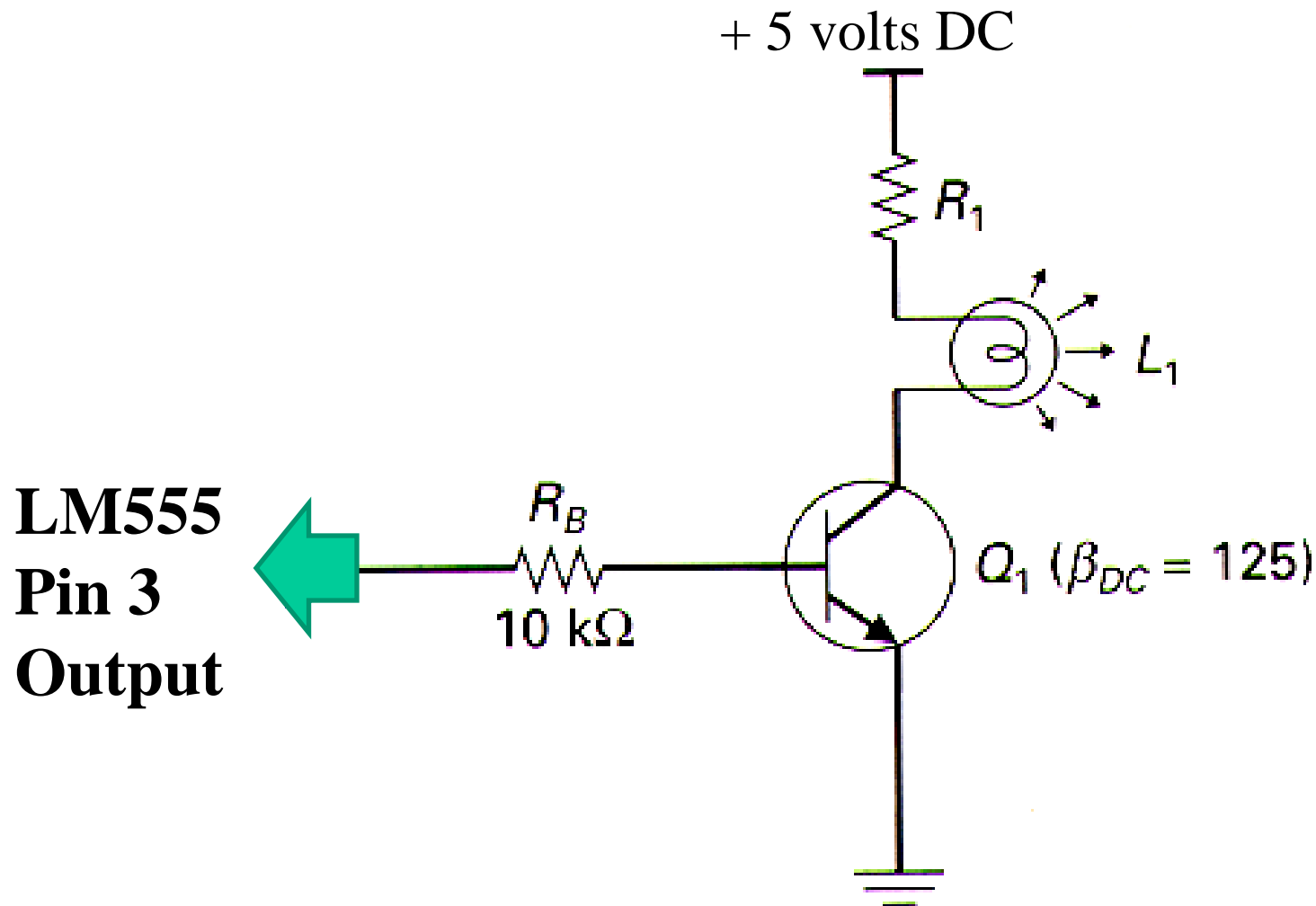

DEVICE: 2N3903 and 2N3904—NPN Silicon Switching and Amplifier Transistors

Maximum continuous
collector current (I_C) = 200 mA.

MAXIMUM RATINGS


Rating	Symbol	Value	Unit
Collector-Emitter Voltage	V_{CEO}	40	Vdc
Collector-Base Voltage	V_{CBO}	60	Vdc
Emitter-Base Voltage	V_{EBO}	6.0	Vdc
Collector Current — Continuous	I_C	200	mA dc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/ $^\circ\text{C}$
*Total Device Dissipation @ $T_C = 25^\circ\text{C}$ Derate above 25°C	P_D	1.5 12	Watts mW/ $^\circ\text{C}$
Operating and Storage Junction Temperature Range	T_J, T_{stg}	-55 to +150	$^\circ\text{C}$

*THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	$^\circ\text{C/W}$
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	$^\circ\text{C/W}$

2N3903
2N3904★


CASE 29-04, STYLE 1
TO-92 (TO-226AA)

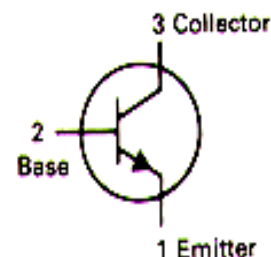

GENERAL PURPOSE
TRANSISTORS


NPN SILICON

PWM Lamp brightness voltage control

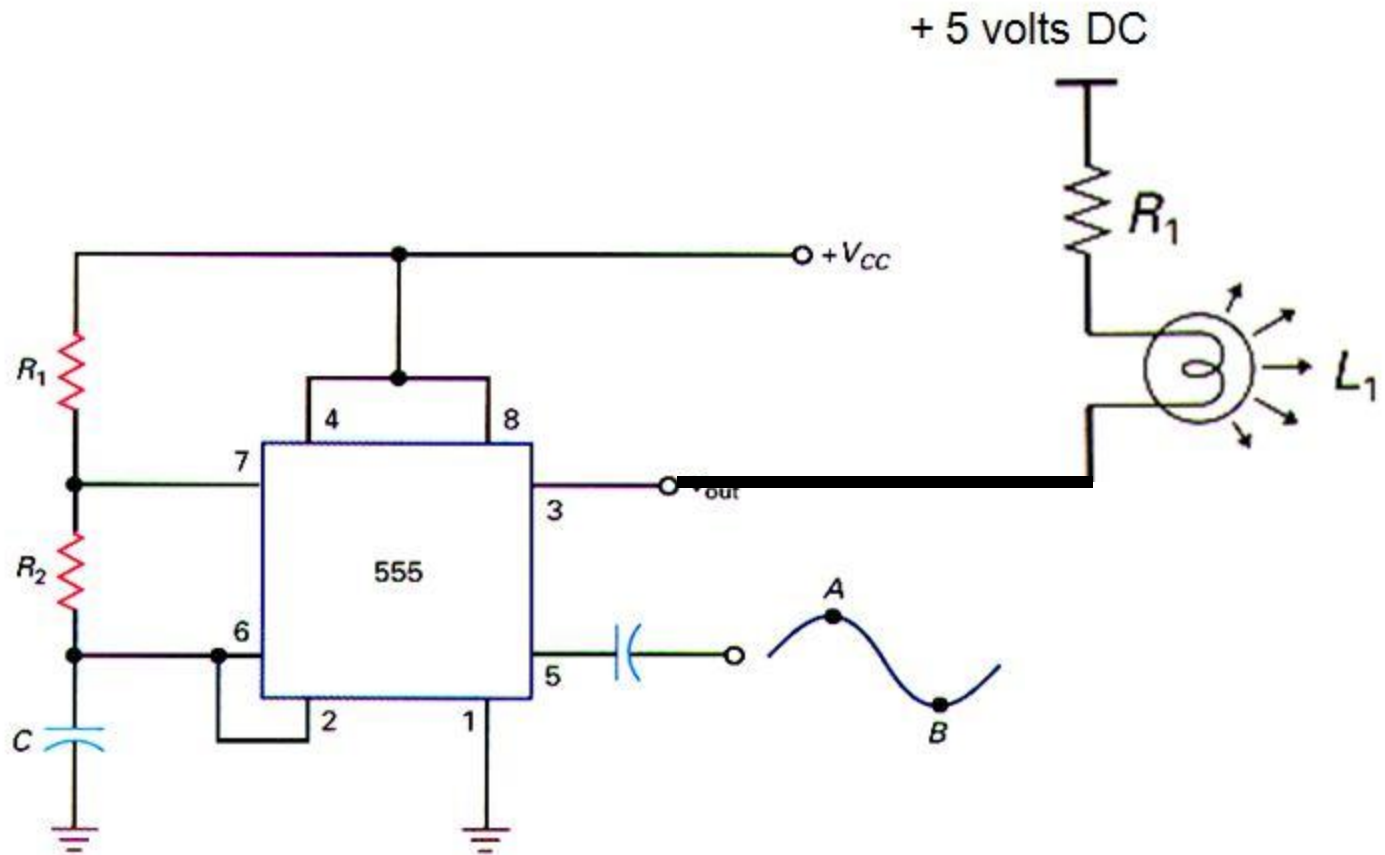

(a)

Pulse - Position Modulator

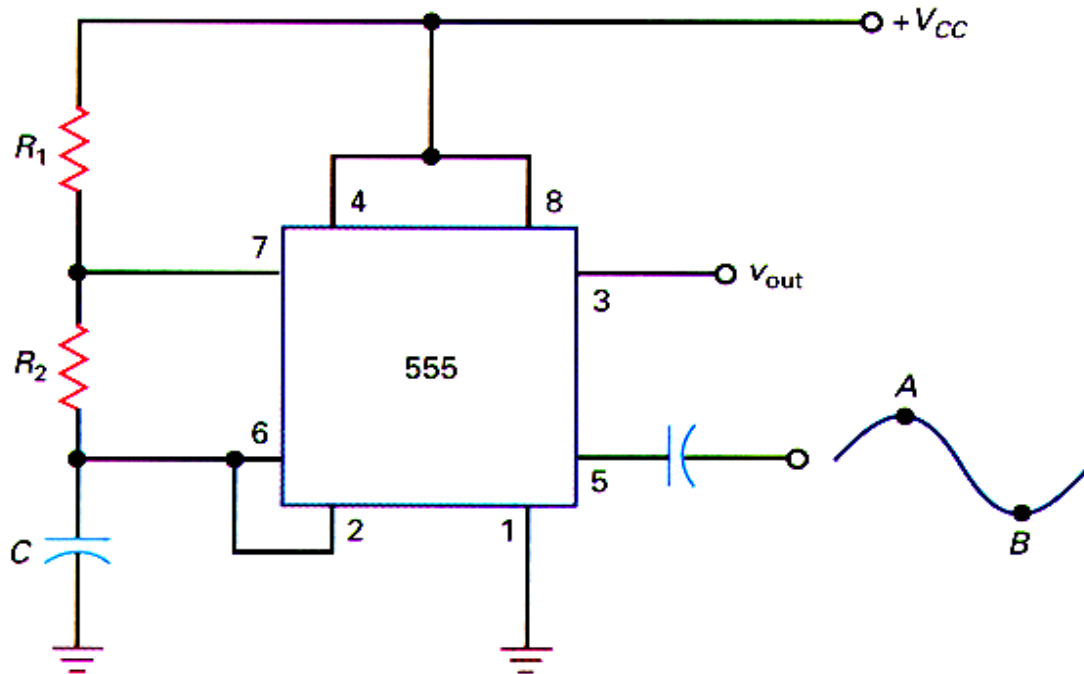


(a)

$$UTP = \frac{2V_{CC}}{3} + v_{mod}$$


$$W = -(R_1 + R_2)C \ln \frac{V_{CC} - UTP}{V_{CC} - 0.5UTP}$$

$$T = W + 0.693R_2C$$

$$\text{Space} = 0.693R_2C$$

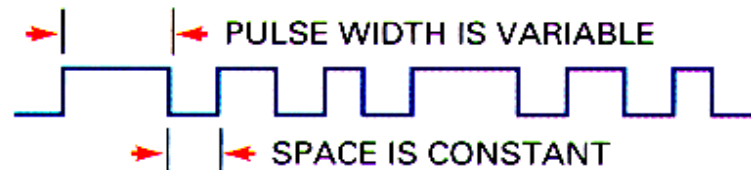


Analog Discovery Design Kit

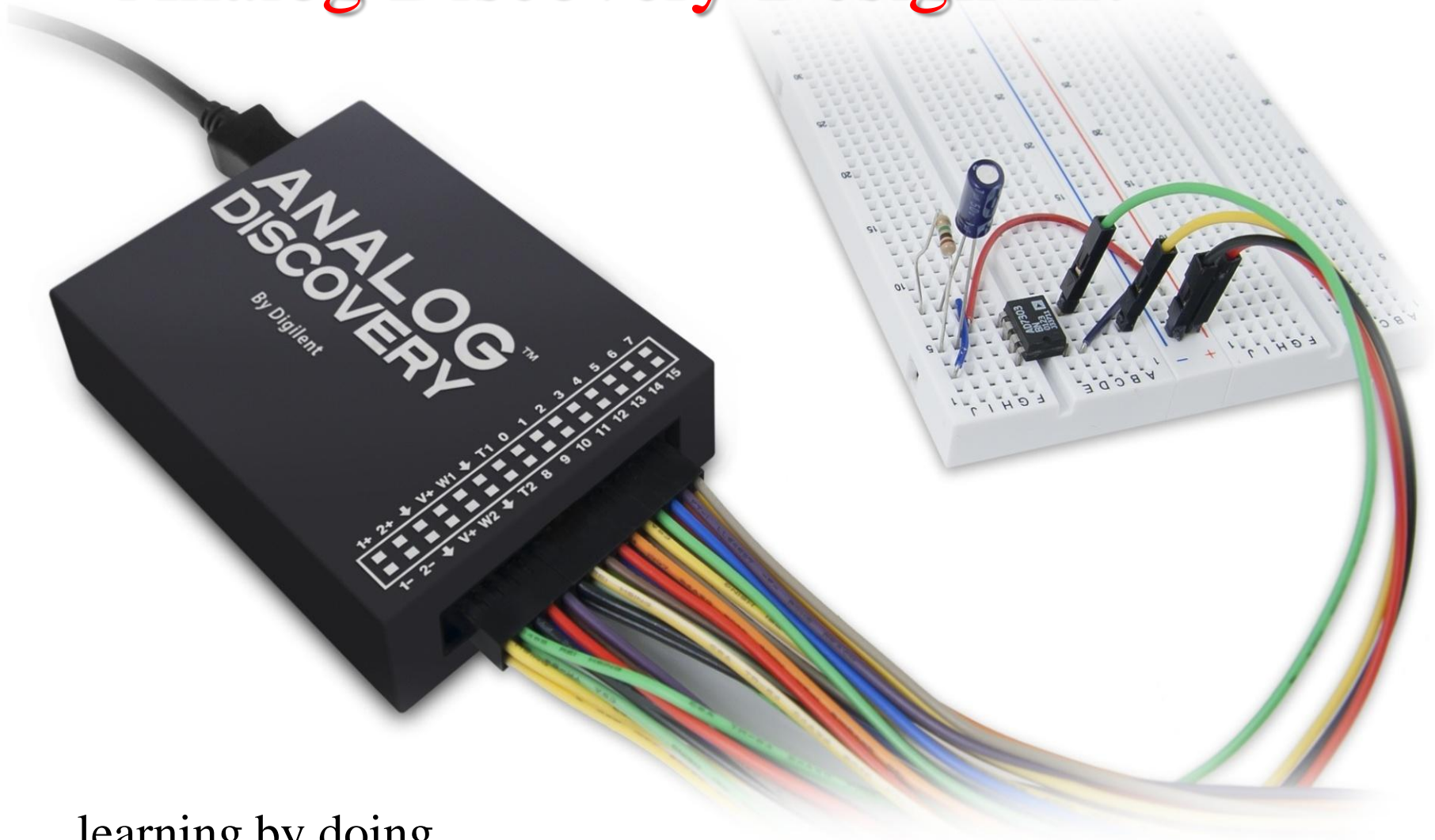


learning by doing

U-Mass, Alan Rux


Leads we will be using today

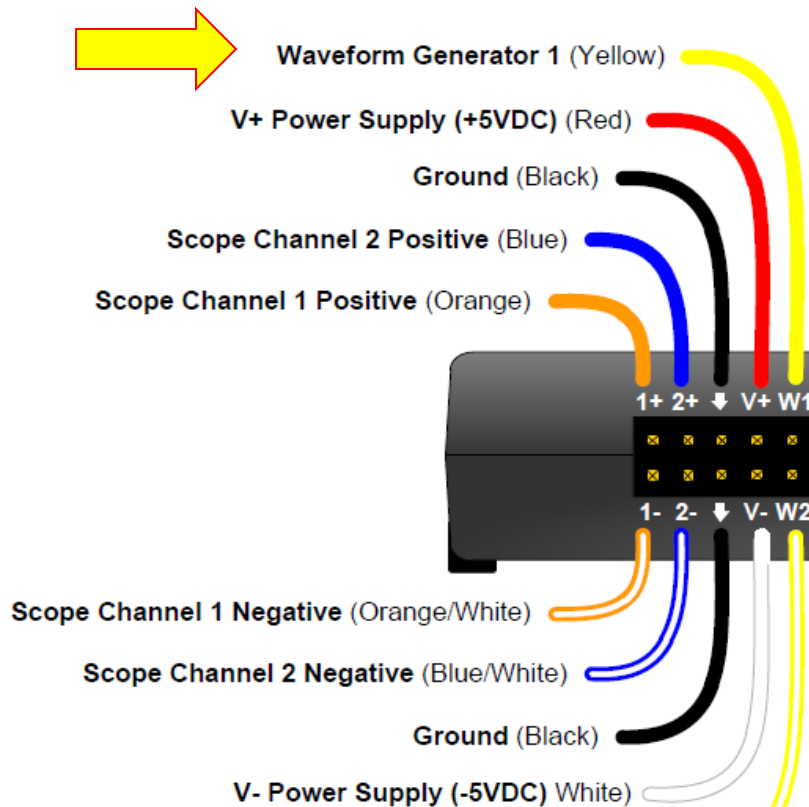

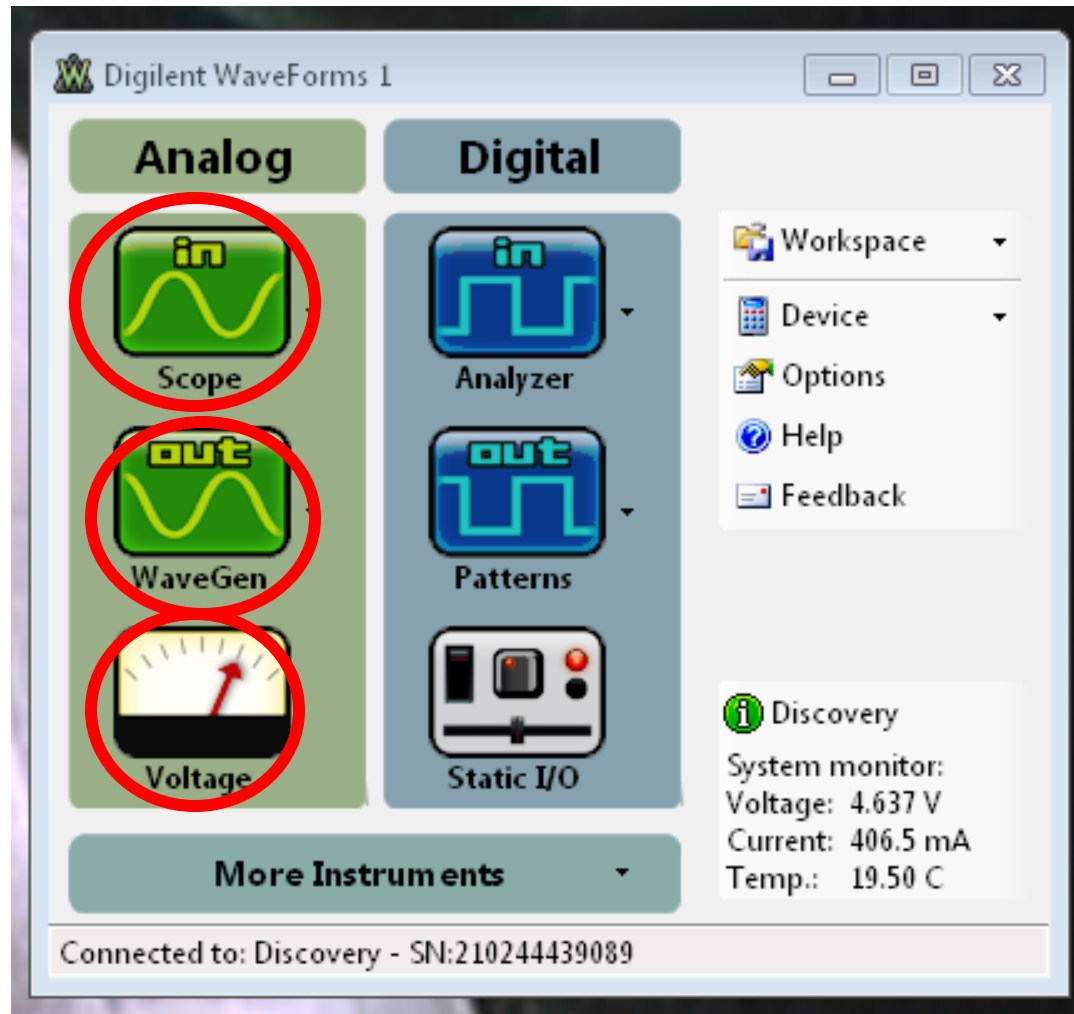To enable the oscilloscope click on the
“Scope - in” icon






2 Channel Oscilloscope Window

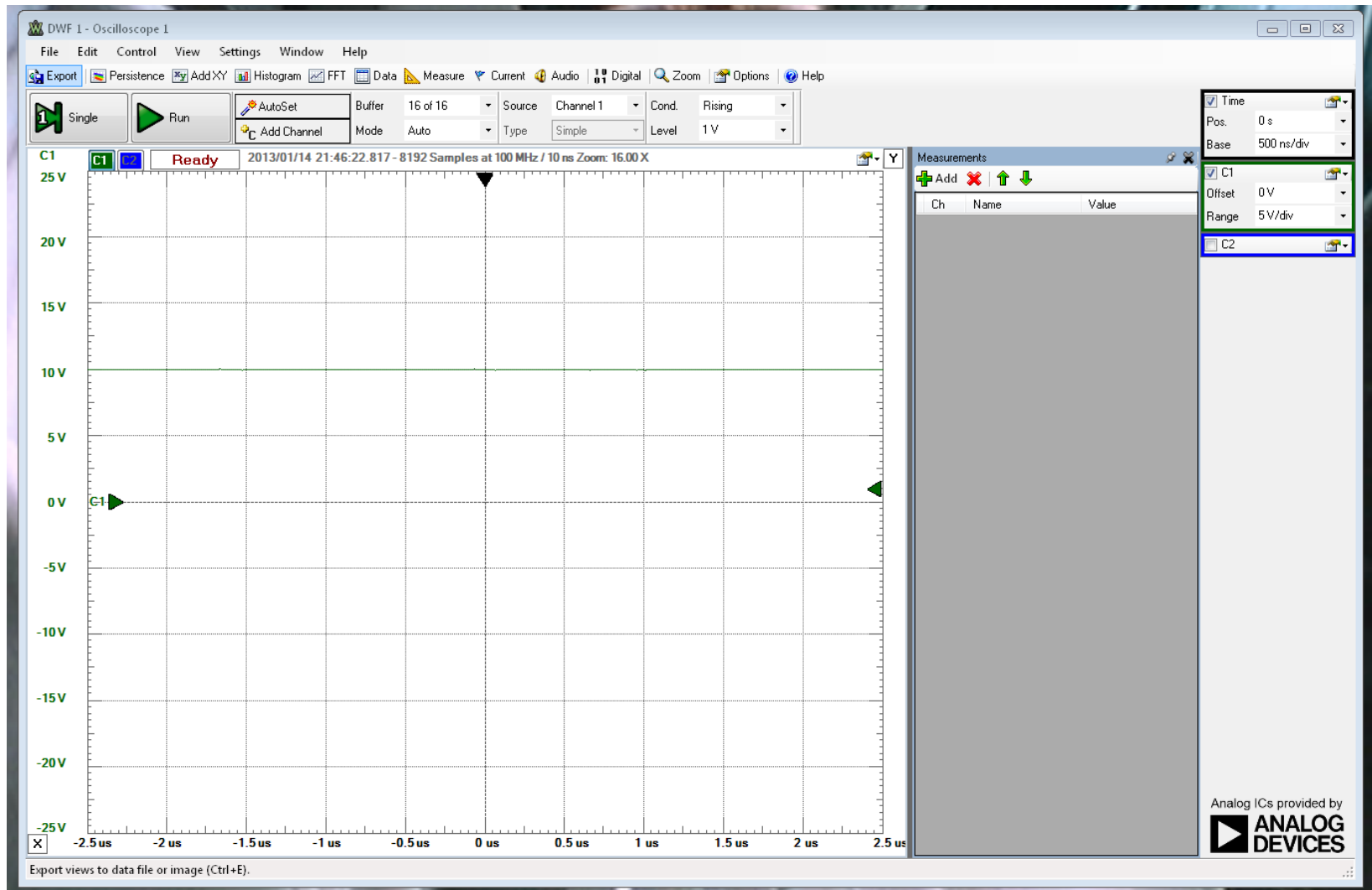

Waveform Generator Window

1 Channel, AWG-1

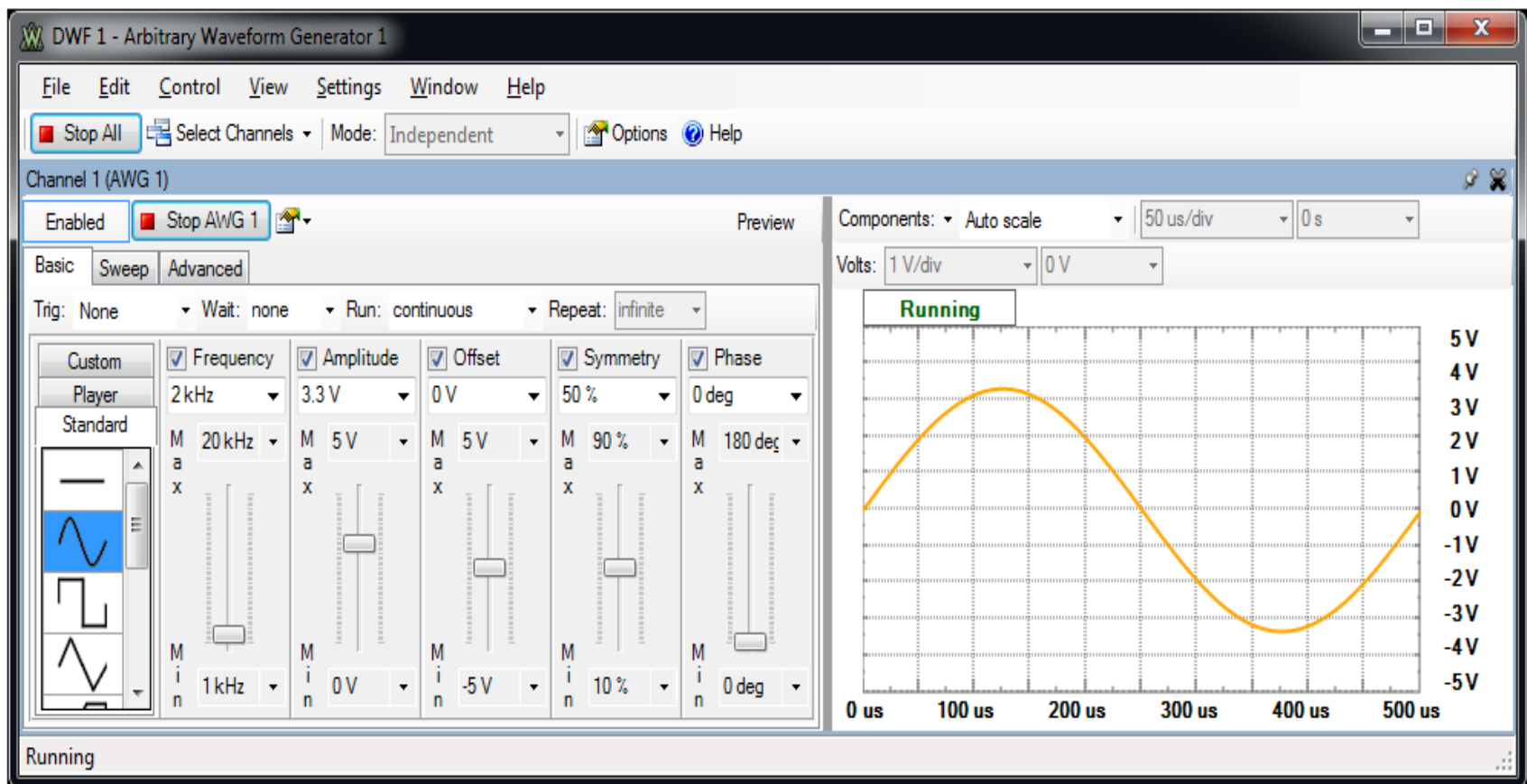


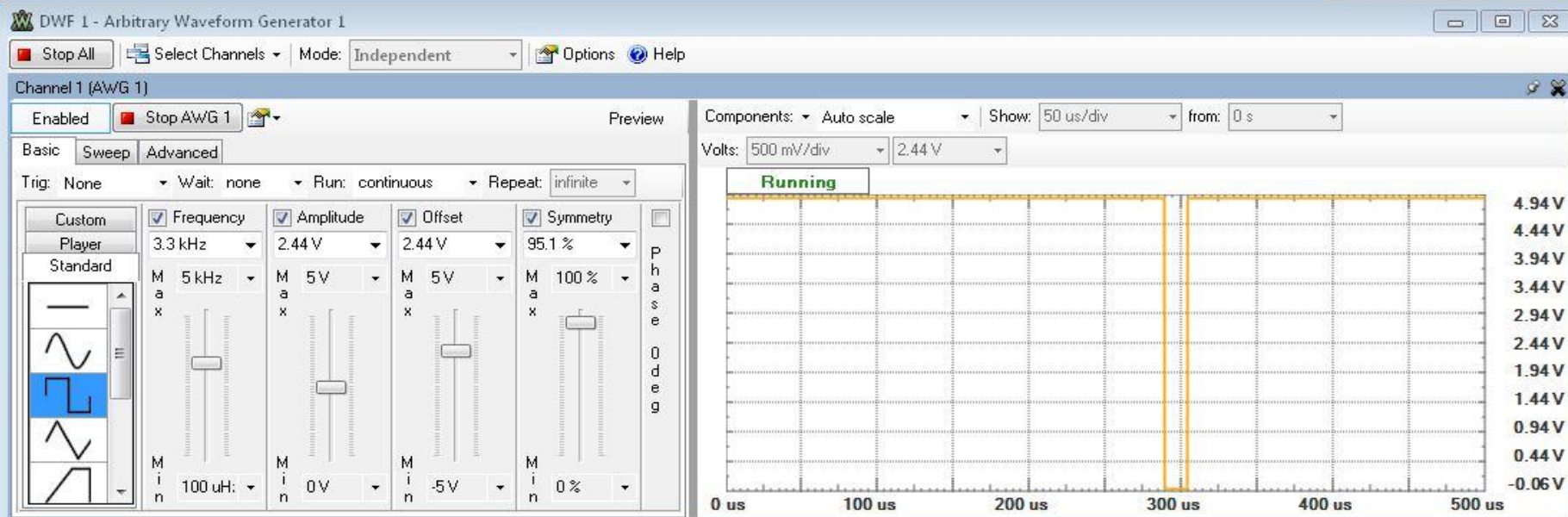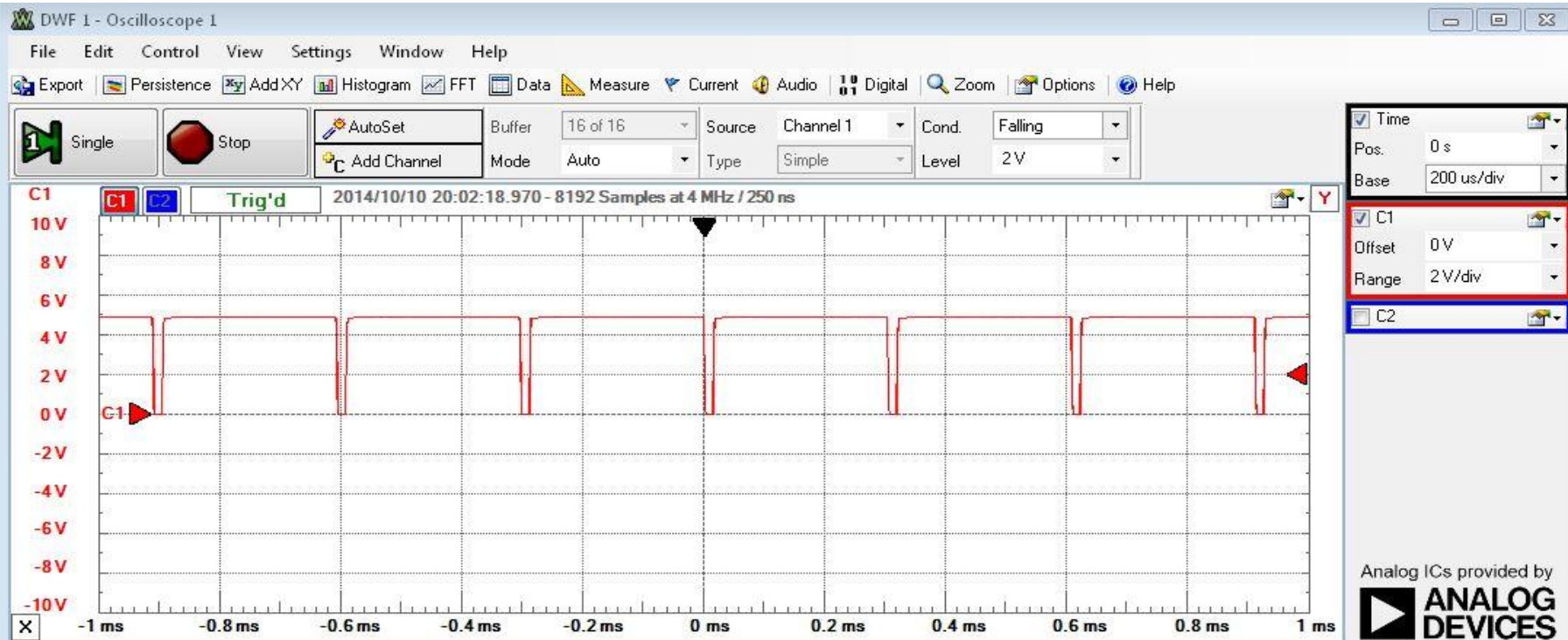

DIY_{ASDE}

- Take a 555 running a square wave out with 50 / 50% duty cycle
- Pass the sq. wave through an integrator circuit, need offset on op-amp if using single voltage source, LM324 op-amp.
- Pass integrated triangular wave through op-amp shaping circuit = sine wave, offset also required with single voltage supply

Astable Operation (free-run)

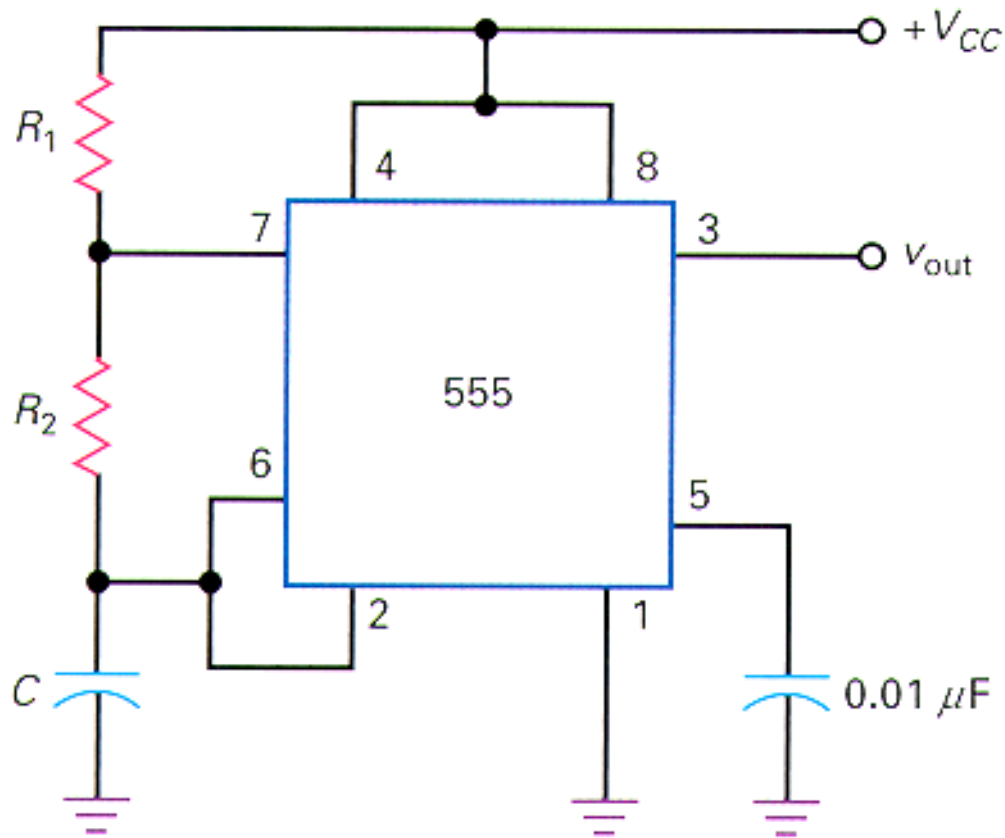


$$W = 0.693(R_1 + R_2)C$$

$$T = 0.693(R_1 + 2R_2)C$$


$$f = \frac{1.44}{(R_1 + 2R_2)C}$$

$$D = \frac{R_1 + R_2}{R_1 + 2R_2}$$

Basic triangular-wave generator.

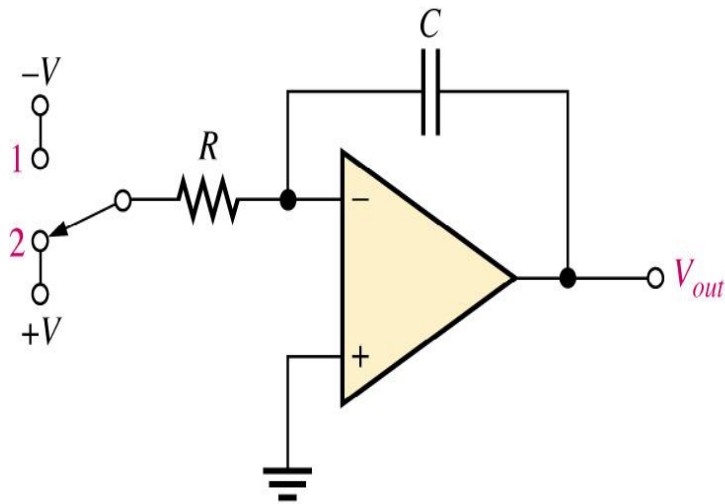


(a)

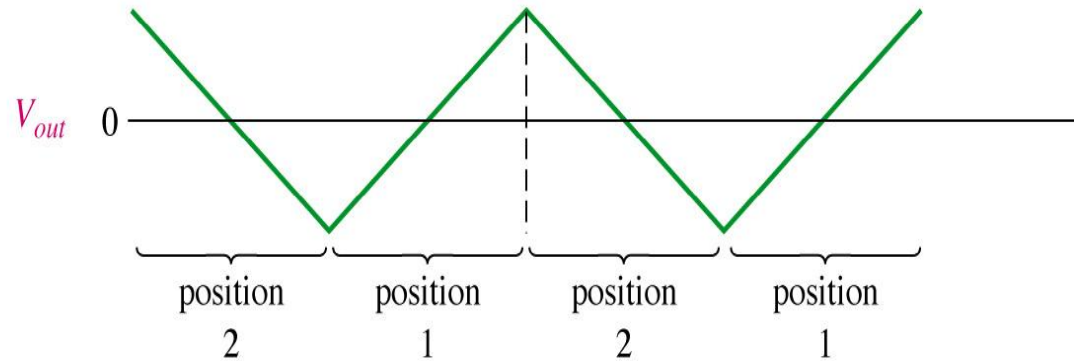


(b) Output voltage as the switch is thrown back and forth at regular intervals

Square wave to triangular wave

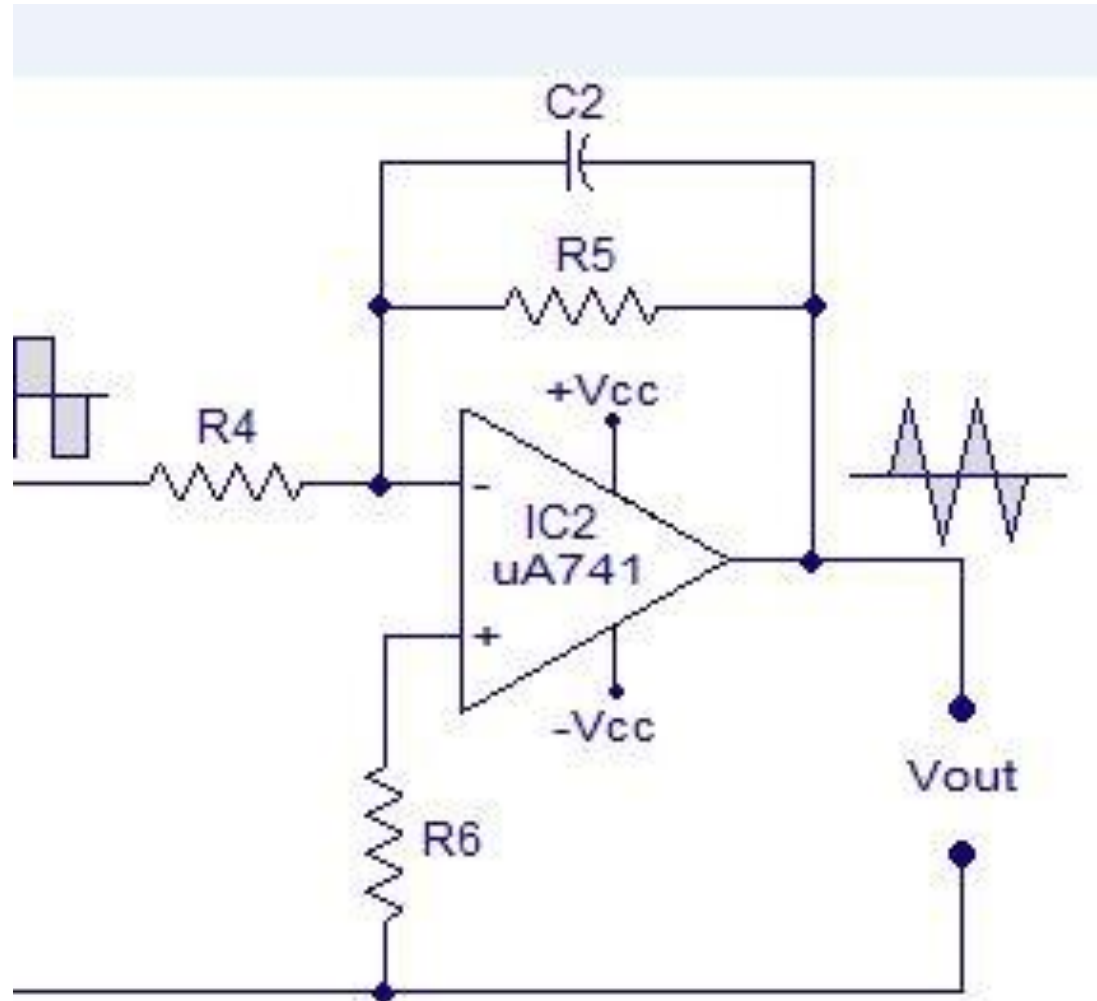

Triangular wave to Sine wave

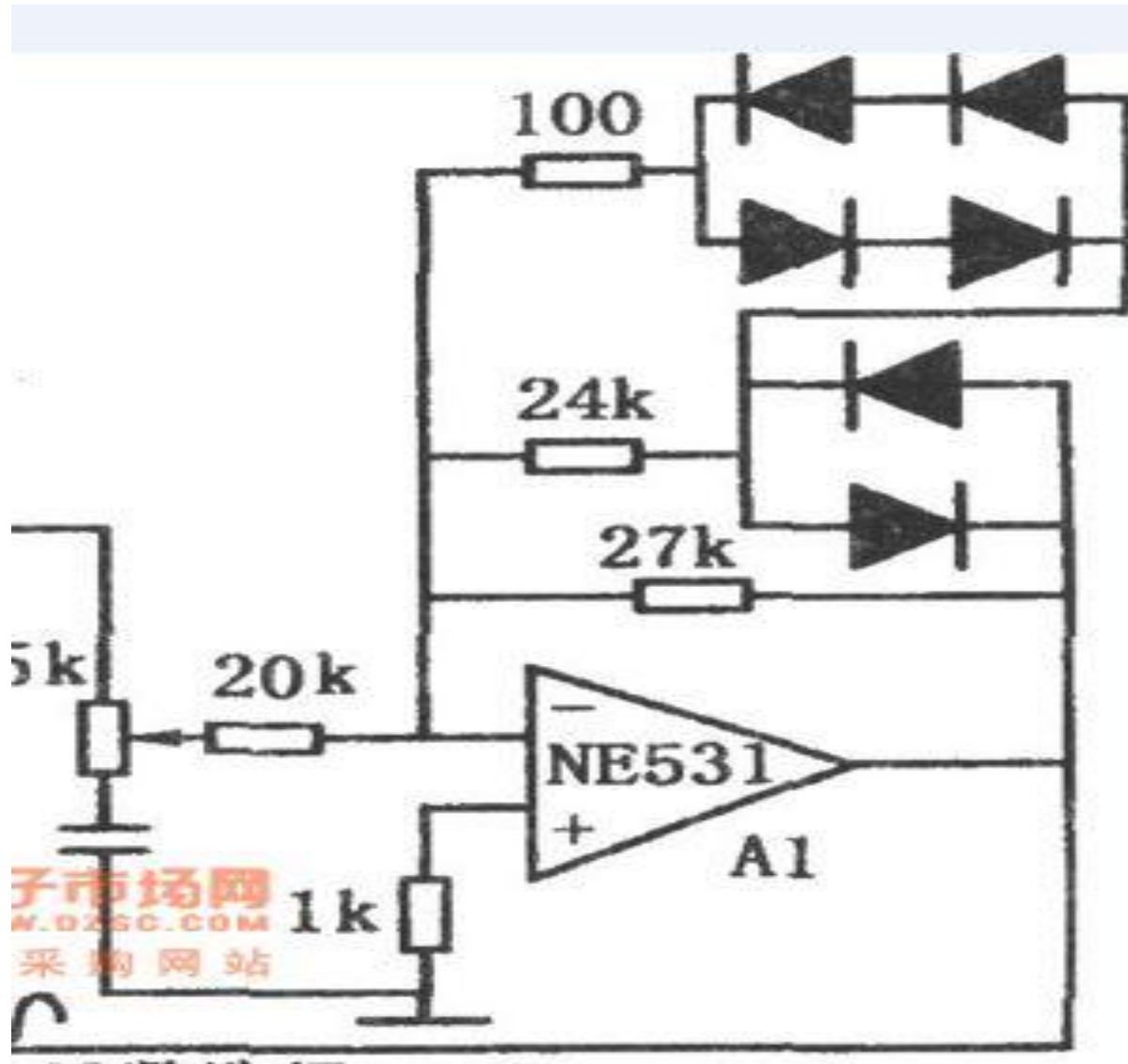

*Let the **Fun** & **Learning** Begin*

